


# Ultra Low Power Analog Integrated Circuits for Implantable Medical Devices

Fernando Silveira

Universidad de la República, Uruguay



CCC Medical Devices  
nanoWattICs

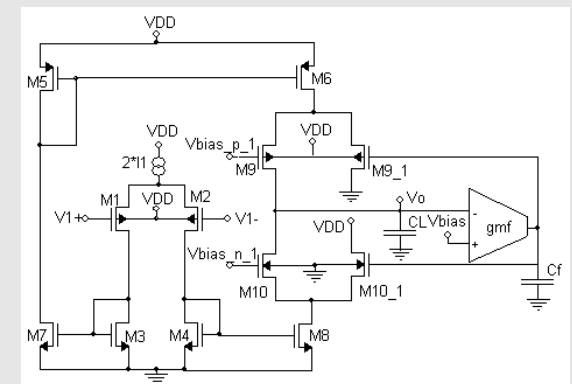

# Objectives of this talk

- Introduce the needs and characteristics of Active Implantable Medical Devices (AIMDs) from the circuit designer point of view.
- Present the techniques and circuits applied in Analog ULP
  - Device Modeling
  - Design Methodology
  - Circuit techniques
- Show the current research and development topics and prospects of the area

# Engineering School

## Universidad de la Republica



Wikipedia



Wikipedia



Collins/Fing

Montevideo

- Founded 1888, approx. 1k new students / year, 670 teaching staff

# Microelectronics Group

- Since 1991
- Under Graduate & Graduate Teaching (MSc, PhD)
- Research
  - Design of Analog / RF and Mixed-Signal Integrated Circuits, particularly Ultra-Low Power (ULP)
  - Also works on ULP Digital / DC-DC and Embedded
- Industrial Experience
  - Implantable Medical Devices
- **2007: spin-off: NanoWattICs**

# Implantable Devices in Uruguay

**Feb. 3, 1960:** Drs. O. Fiandra and R. Rubio performed the first effective pacemaker implant to a human being in the world.

**1969:** Dr. O. Fiandra founded CCC to develop and manufacture pacemakers



**1999:** CCC develops a pacemaker line based on an ASIC designed by the Microelectronics Group of Universidad de la Republica

**Today:** CCC designs and manufactures active implantable devices and complete medical systems for third parties.

# Outline

- I. System: Active Implantable Medical Devices Today
- II. Transistors and Circuits: Analog Design for ULP.
  - Transistor Modeling.
  - Design Methodology.
- III. Circuit Techniques: Implementation of AIMDs blocks
- IV. Conclusions and Prospects

# Active Implantable Medical Devices (AIMD)

- Implantable: Introduced **inside the body** by a medical procedure and **intended to remain there** after the procedure.
- Active: Including a Power Source
- Not considered here:
  - Passive implants (e.g. bone prostheses, valves, stents)



# Portable, Wearable, Swallowable Medical Devices ...



[www.givenimaging.com](http://www.givenimaging.com)

<http://mobilewellbeing.wordpress.com/>



# AIMDs: Main Historical Milestones (I)

- Cardiac Pacemaker: first implantable device, 1960




- Cochlear Implants (1960s -)




# AIMDs: Main Historical Milestones (II)

- Cardiac Defibrillators (1980)

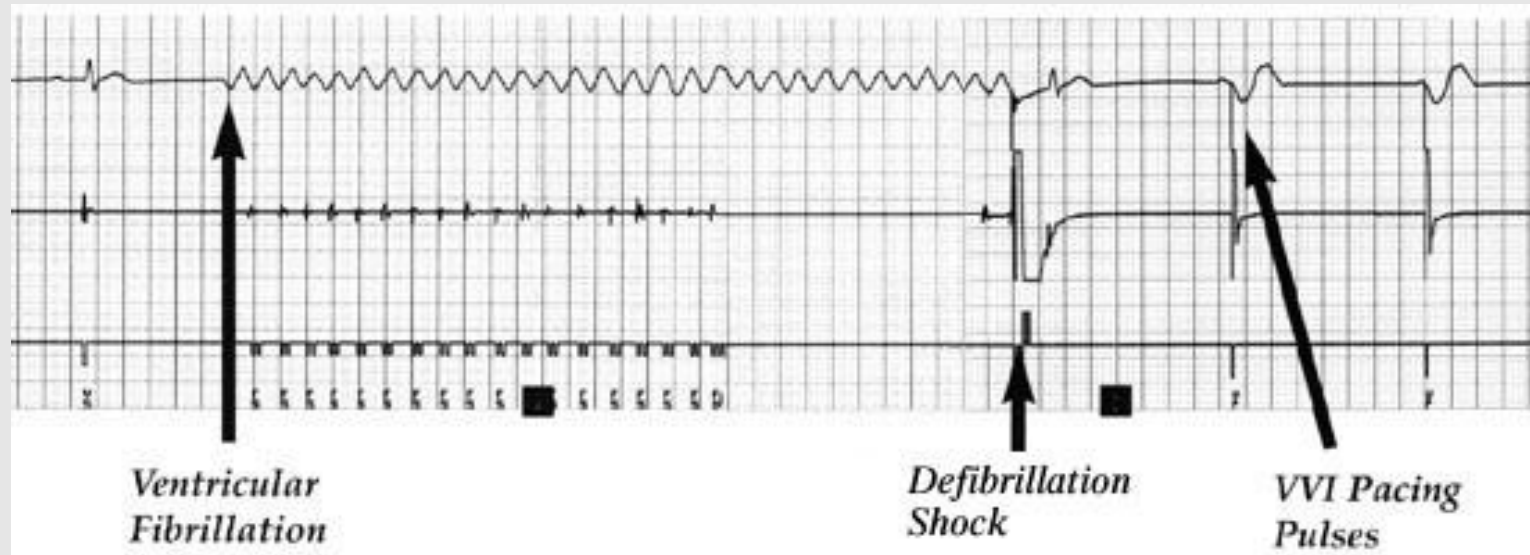

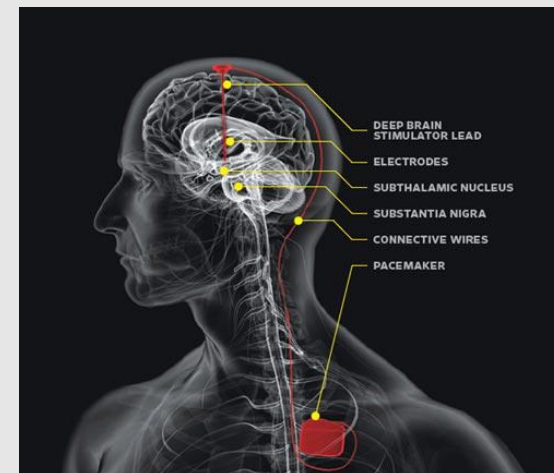- Deep Brain Stimulator for Parkinson (1995)



# AIMDs: Some of the new developments

- Heart Failure
- Obesity
- Diabetes
- Neurostimulators:
  - Pain control
  - Blood pressure control
  - Foot drop correction
  - Urinary incontinence
  - Sleep Apnea
  - ...
- Patient monitoring
- Brain – computer interface



# Some system examples

- Pacemaker:
  - **Goal:** Treat Bradycardia (slow heart rhythm) and conduction disorders between atria and ventricles
  - **How:** Stimulating to contract the heart when it does not contract spontaneously (“watchdog”)
  - **Sensing of:**
    - cardiac muscle signals that indicate ventricles / atria contraction
    - other indicators of physical activity, additionally in some cases

# Basic Functions



- Stimulation (Open Loop)
  - Early Pacemakers
  - Cochlear Implants
  - Deep Brain Stimulators for Parkinson
  - Neurostimulators (sometimes “Man/Woman in the loop”)
- Stimulation and Sensing (Closed Loop)
  - Cardiac area (Pacemakers, Defibrillators, Heart Failure)
  - Obesity
  - Some Neurostimulators
- Only Sensing
  - Implanted “long term Holter” (“insertable loop recorder”)
- Sensing + external actuation: Brain-computer interface

# Stimulation: Voltage mode

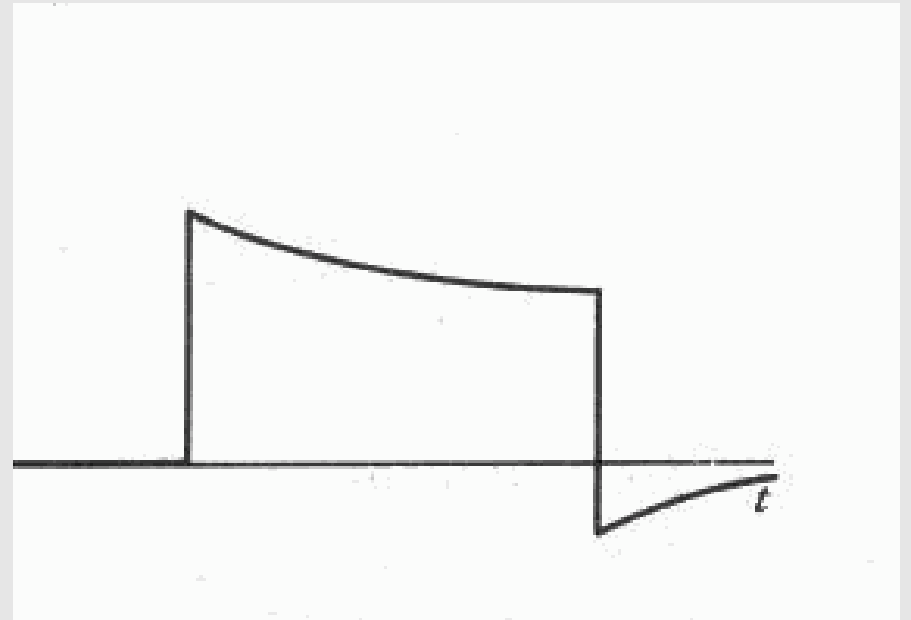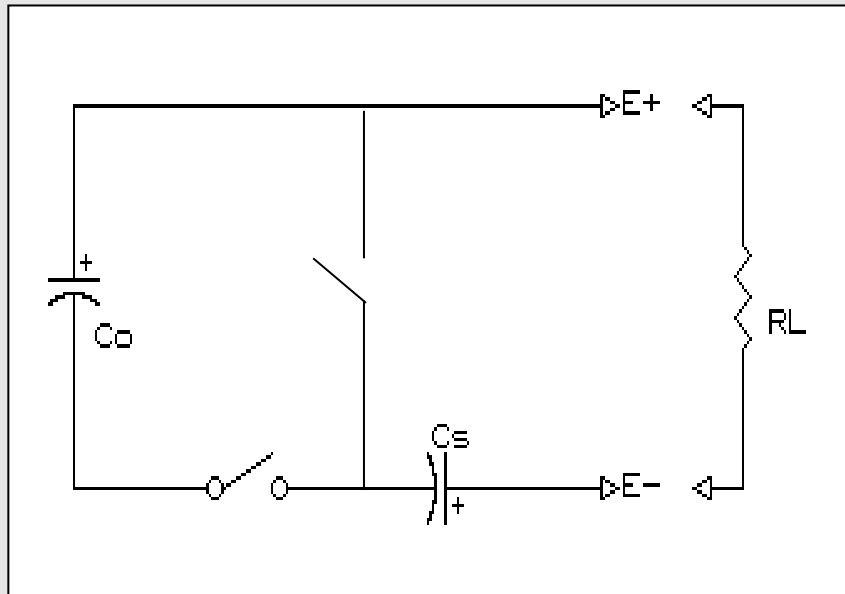

- E.g.: Pacemakers
- 0.1V ... 7.5V
- 50 $\mu$ s ... 1.5ms
- Requires battery voltage multiplier.
- $R_L$ : 500 Ohms typ.

# Stimulation: Current mode

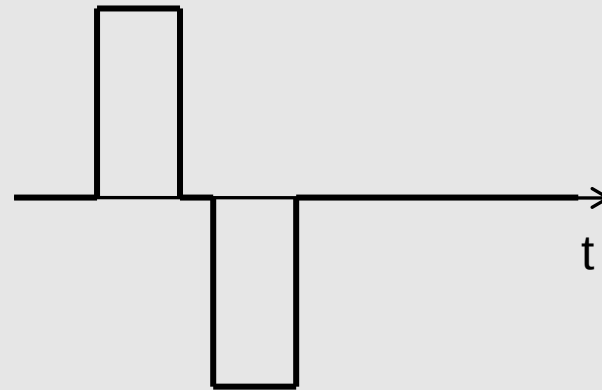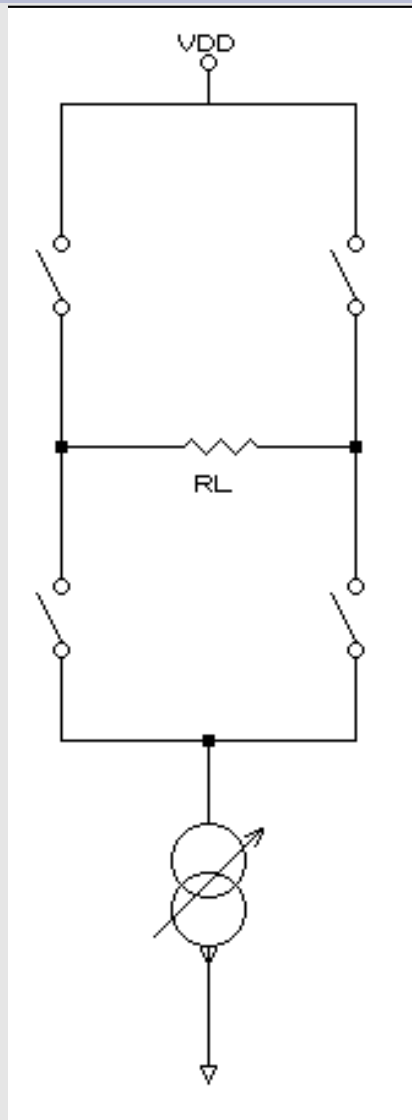

- Neurostimulators and others
- 0.1mA ... 10mA
- 30 $\mu$ s ... 300 $\mu$ s
- Load voltages up to 15V => Requires battery voltage multiplier

# Sensing: Medical signals in general

- **Low frequency:** from  $< 1$  Hz to a few kHz (neural signals)
- **Low amplitude:**  $\mu\text{V}$  to  $\text{mV}$
- **Variability:**
  - " Most measured quantities vary with time, even when all controllable factors are fixed. Many medical measurements vary widely among normal patients, even when conditions are similar " (Source: J. Webster, *Medical Instrumentation. Application and Design*).



Objective of most analog signal processing: qualitative detection for closed loop control.



Traditionally advantage to **analog** implementation in terms of consumption, process scaling is changing this

# Sensing


- Biopotentials:
  - mиеlectric signals (mVs, 100s Hz - 1kHz)
  - cardiac signals (mVs, 10s Hz – 300Hz)
  - neural signals ( $\mu$ Vs, up to 8kHz)
- Impedance (tens of mOhms =>  $\mu$ Vs, few Hz)
- Movement (Physical activity, position) => accelerometer ( $\mu$ Vs (sensor dependent), up to 10Hz)

# Auxiliary Functions

- Telemetry
  - Inductive (up to 10cms)
  - 403 MHz MedRadio Band (a couple of meters)
- Battery Supervision (Voltage / Impedance / Consumed Charge Measurement)
- Lead Impedance Measurement
- Magnet Sensor (Reed Relay / Hall Sensor)
- Battery Recharge (if applicable)
- Control: Microcontroller & Firmware


# Non-implantable System Components

## Medical System Components

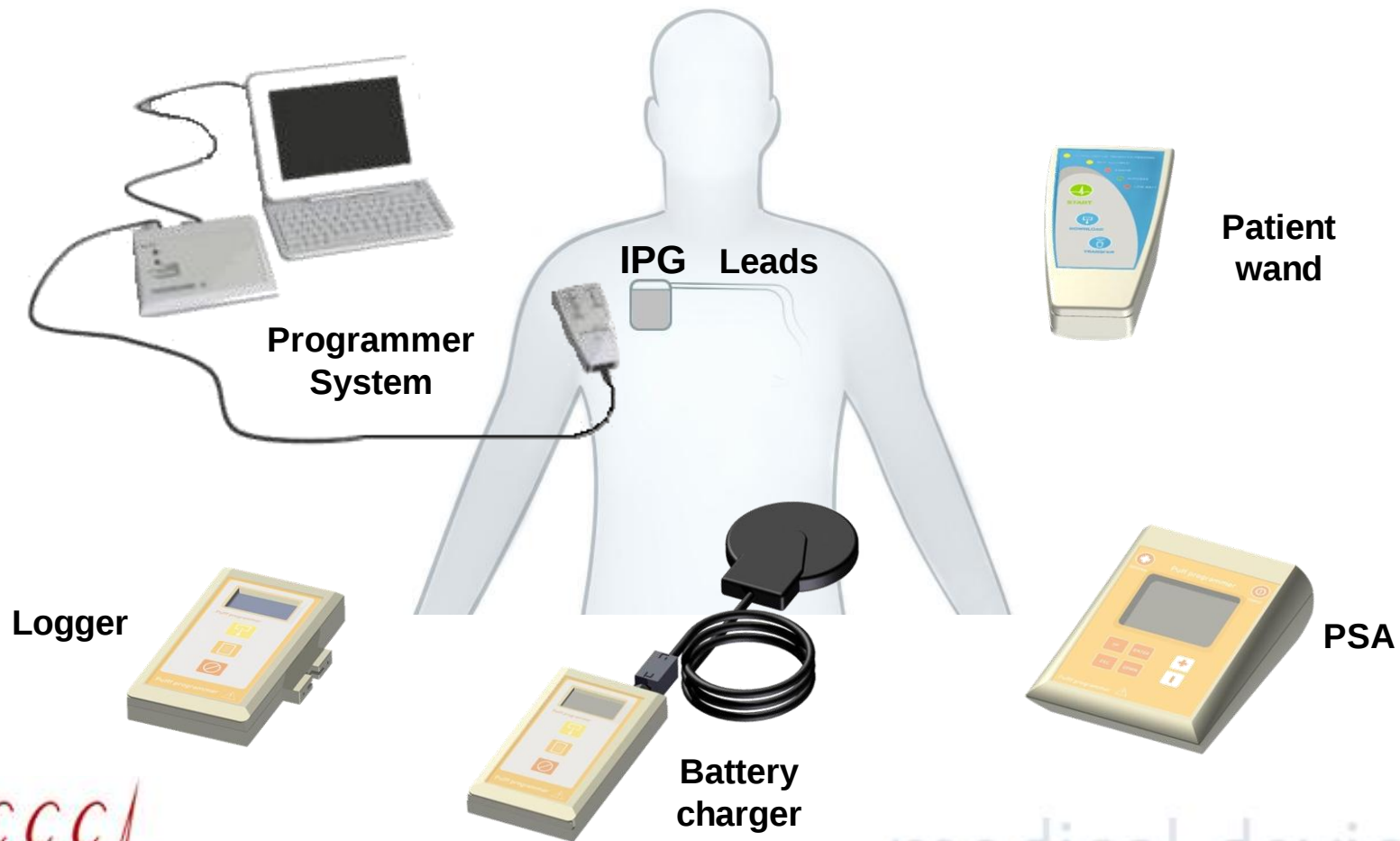

# Example: Implantable Pacemakers


*Approx. Consumption Distribution*

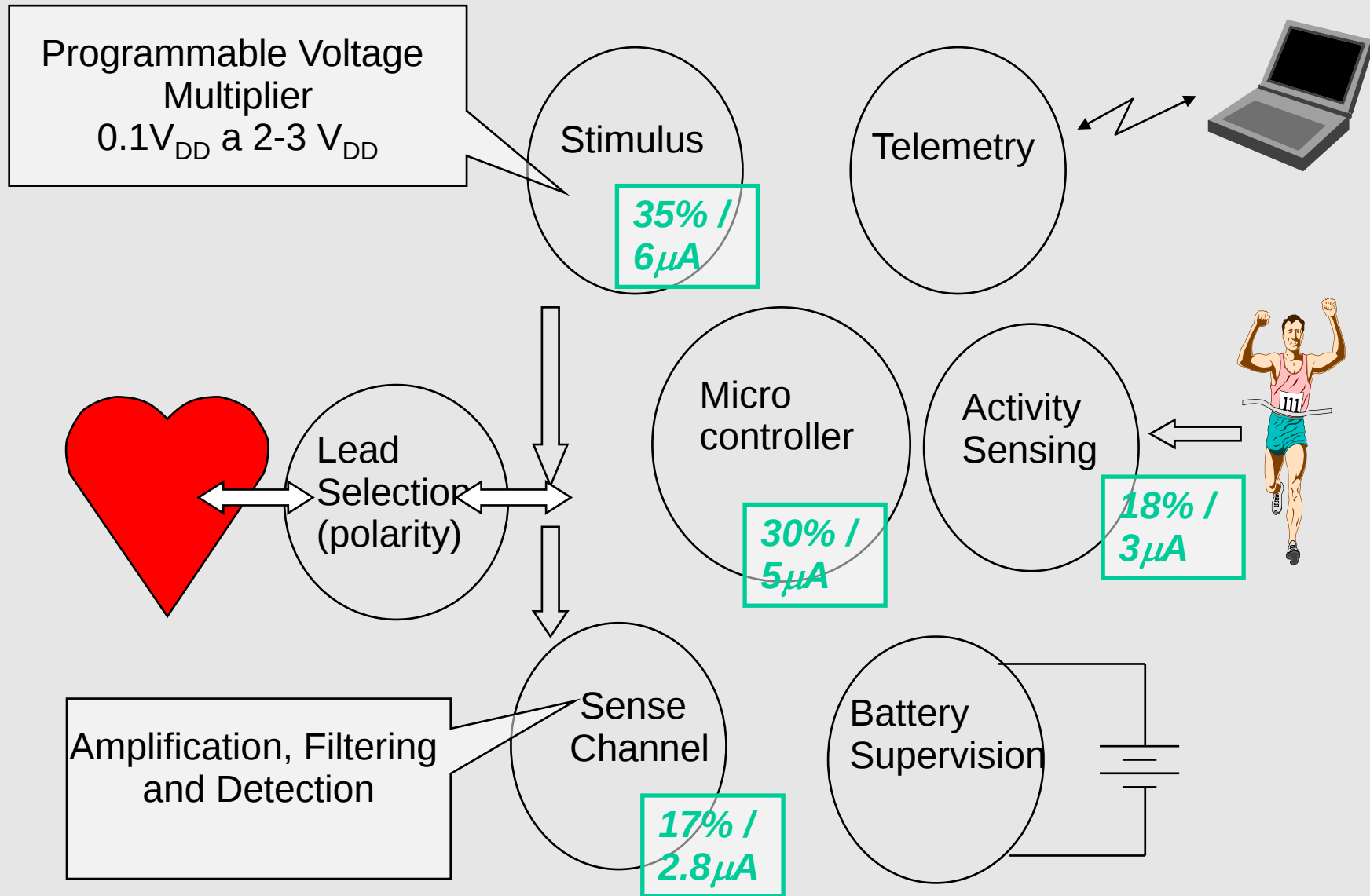

# Example: Closed Loop Stimulator for Drop Foot Correction (I)

- Neurostep System (Simon Fraser Univ, Canada, Neurostream Technologies)
- Closed loop operation based on neural signal sensing and neural stimulation
- On clinical trials
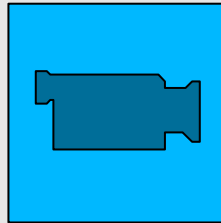
# Example: Closed Loop Stimulator for Drop Foot Correction (II)



<http://www.youtube.com/watch?v=xH2vNu2BbnU>

# General Requirements: Size (and Battery)



Biotronik

1968-  
1998

(Source: M.  
Wilkinson, course:  
MST for Medical  
Devices)



Currently approximately 12 cc (5cm x 4cm x 0.6cm)

Approx. **30 to 40%** occupied by the **battery**

➡ Less consumption = Smaller size @ Equal Service Life

**Consumption internal to the circuit: 50% to 75% of total consumption**

➡ **There is room and need for improvement**


# General Requirements: Power Supply (II)

For higher average consumption devices:

- Rechargeable lithium batteries (since approx. year 2000, capacity in the order of **0.3Ah**)
- Direct powering from RF energy transmitted transcutaneously

# General Requirements: Safety and Reliability

**This is not acceptable !!!**

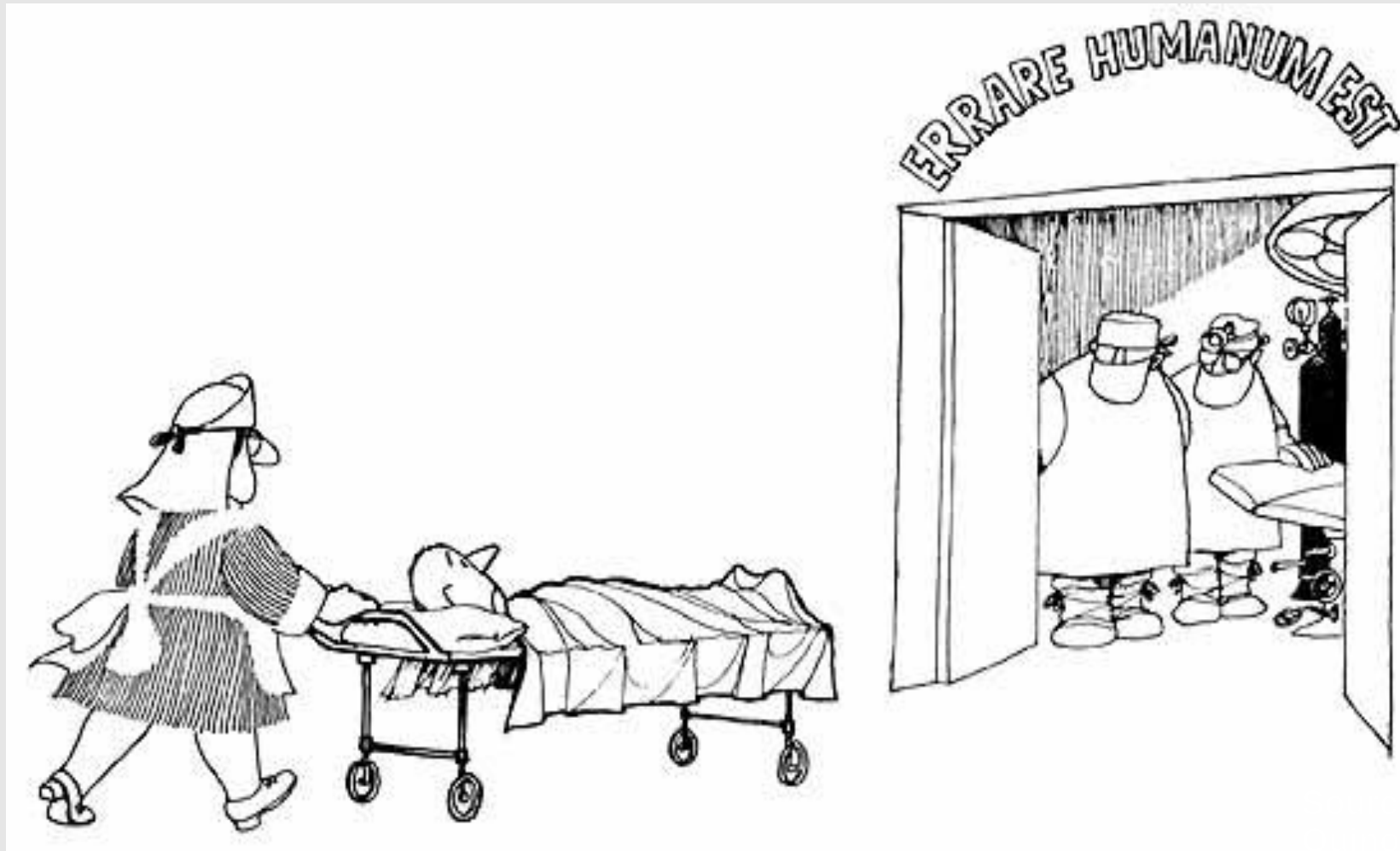

# General Requirements: Safety and Reliability

Reliability => Frequency and probability of faults

Safety: Involves many aspects, particularly:

=> A single fault must not provoke a catastrophic event

**High Reliability** => Probability of single fault is low and double fault is virtually impossible

**+**

**Safety**

=> Probability of malfunctioning is low

=> Catastrophic Failure: virtually impossible

# General Requirements: Safety and Reliability

Involves all the stages:

- System and Circuit Design

- System and Circuit Verification, Qualification and Medical Validation

- Medical Device Application, Configuration and Use

Strongly conditions design: E.g. Limiting DC leakage towards the heart under single fault conditions => external capacitors

Importance of paying attention from the very beginning to applicable standards on AIMD safety, risk analysis and applicable regulations.

# Outline

I. System: Active Implantable Medical Devices Today

II. Transistors and Circuits: Analog Design for ULP.


Transistor Modeling.

Design Methodology.


III. Circuit Techniques: Implementation of AIMDs blocks

IV. Conclusions and Prospects

# MOST Inversion Regimes (1)


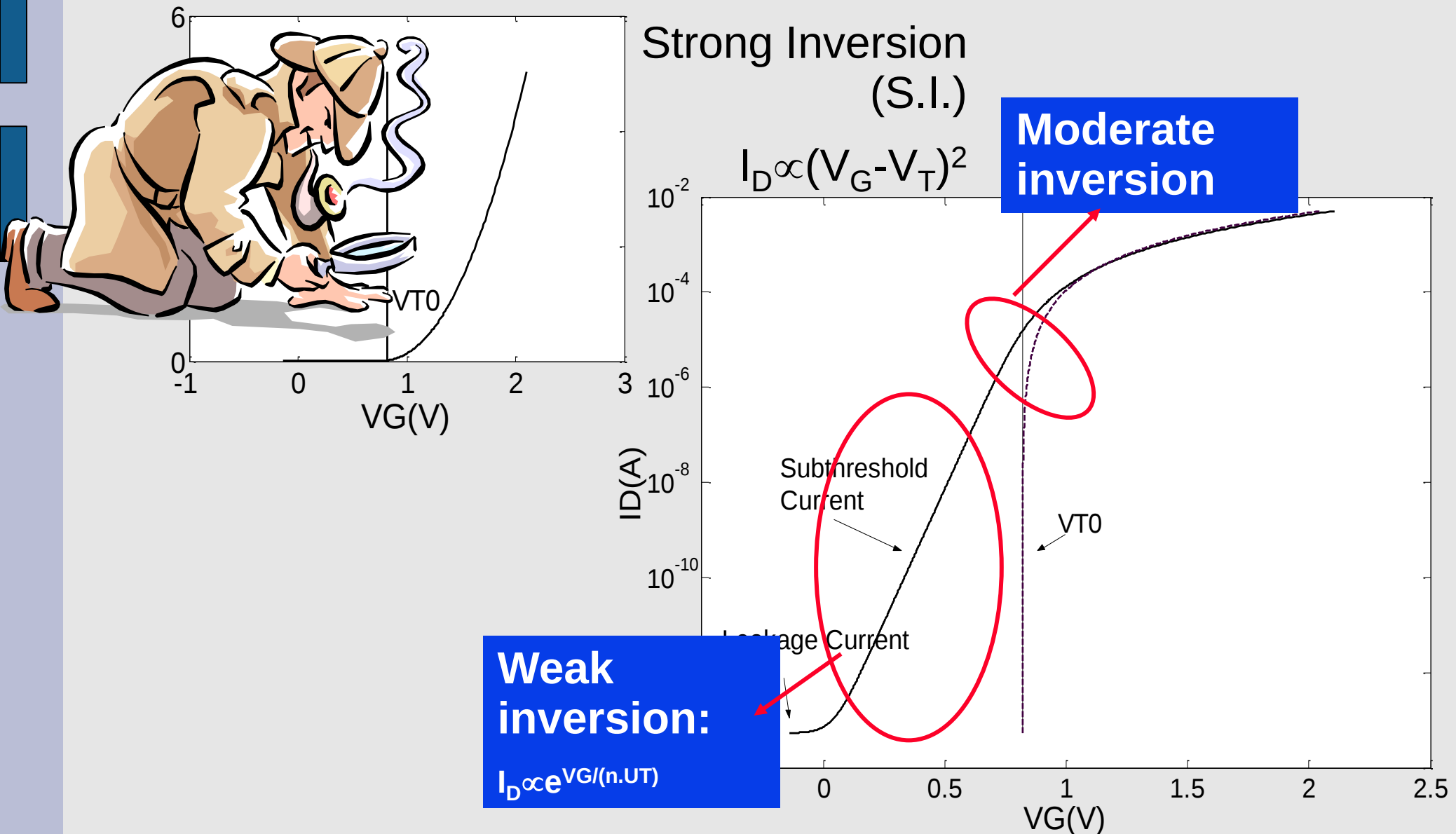


# All regions, continuous MOST models

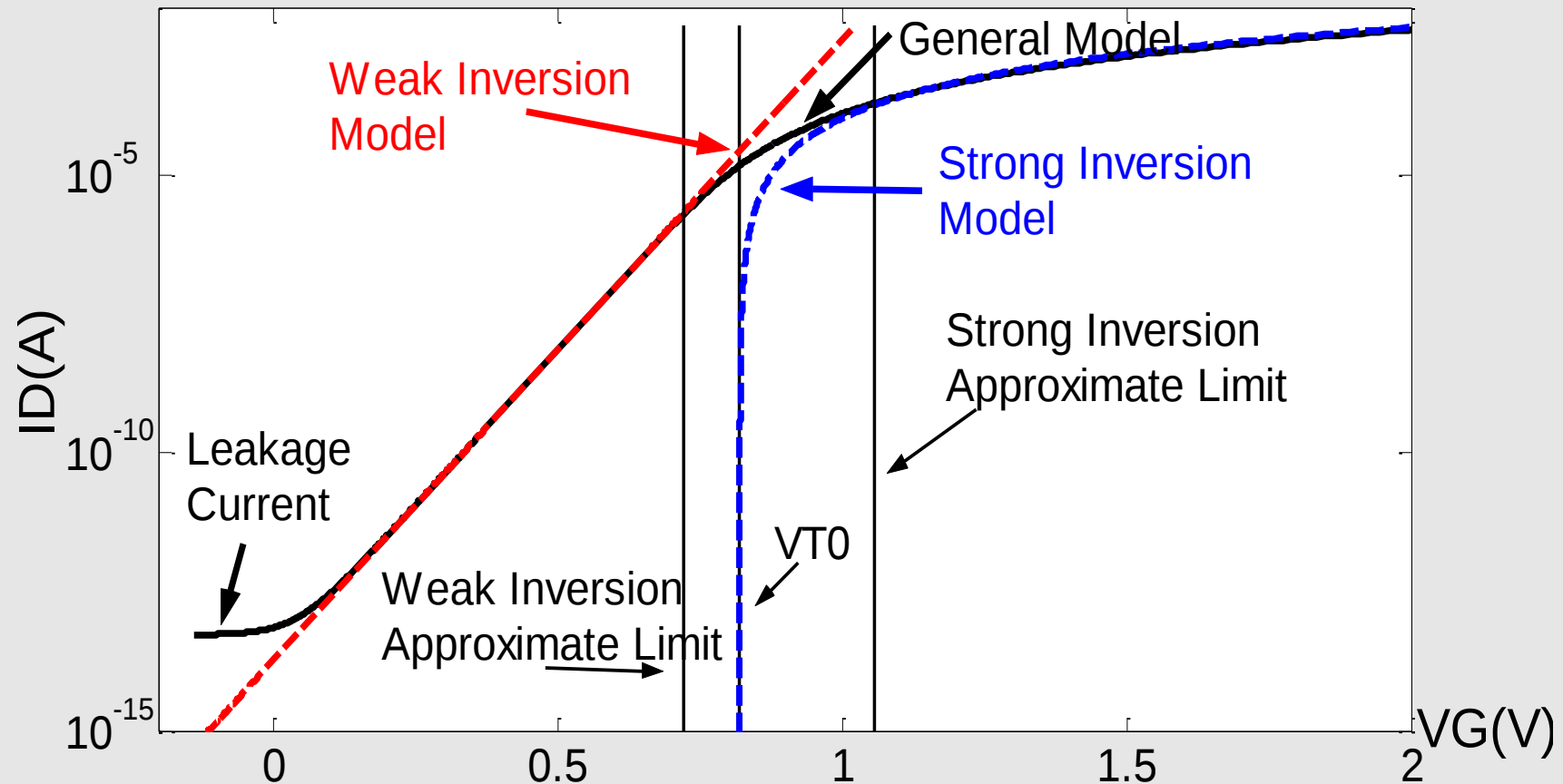

- EKV (Enz, Krummenacher, Vittoz, EPFL, AICSP 1995): originally mathematic interpolation between strong and weak inversion equations, now physical
- ACM (Advanced Compact Model, A. Cunha, C. Galup-Montoro, M. Schneider, UFSC, IEEE JSSC 1998): Physical model.
- ... or **experimental / simulation curves**

# “Intrinsic” MOS Amplifier

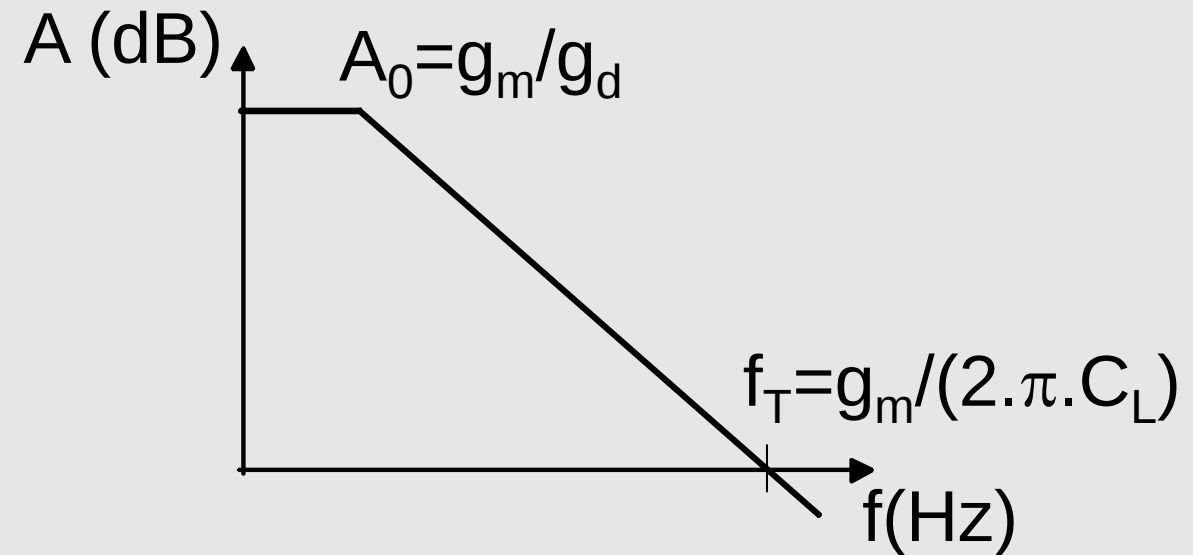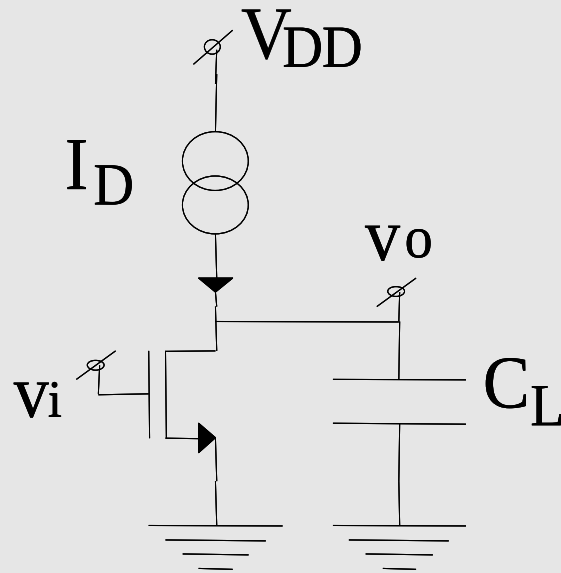

OTA: Operational Transconductance Amplifier

$$A_0 = g_m \cdot r_o = \frac{g_m}{g_d} = \frac{g_m}{I_D} \cdot V_A = \frac{g_m}{I_D} \bigg/ \frac{g_d}{I_D}$$



$$f_T = \frac{g_m}{2\pi C_L}, \quad A = \frac{A_0}{1 + \frac{s \cdot A_0}{2\pi f_T}}$$

- Consumption:  $I_D$
- Speed  $g_m/C_L$
- $C_L$ : total: external + parasitics
- Speed - Consumption trade-off :  $g_m/I_D$

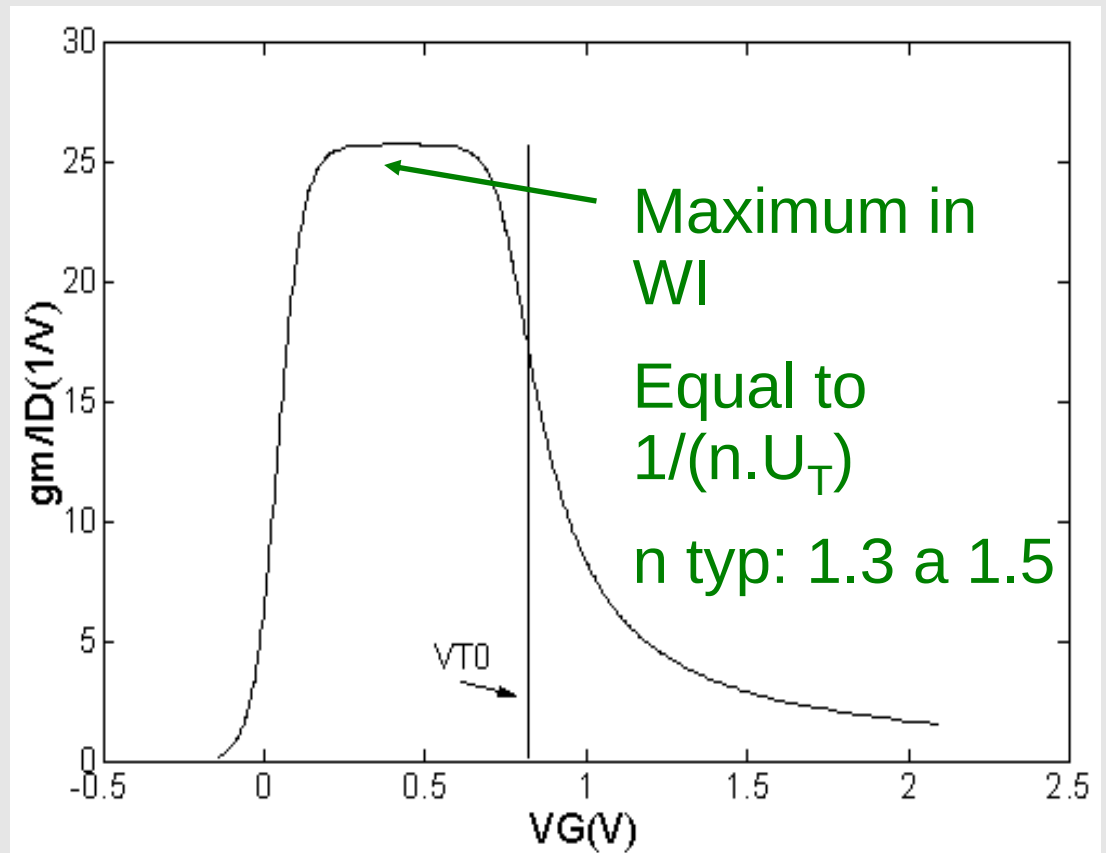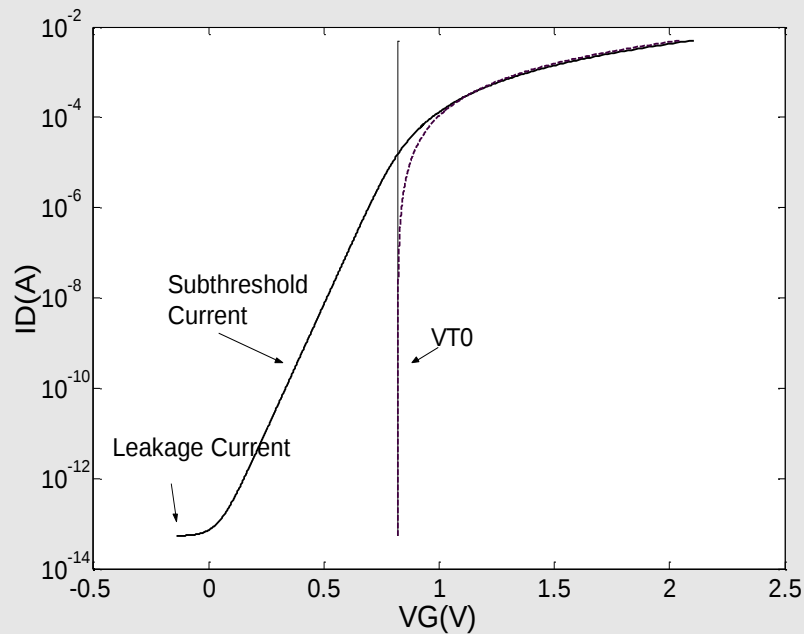
# $g_m/I_D$ vs. $V_G$

$$\frac{g_m}{I_D} = \frac{1}{I_D} \frac{\partial I_D}{\partial V_G} = \frac{\partial \log(I_D)}{\partial V_G}$$

- $g_m/I_D$  is the slope of  $I_D$  vs.  $V_G$  in log scale



## $g_m/I_D$ vs. $I_D$

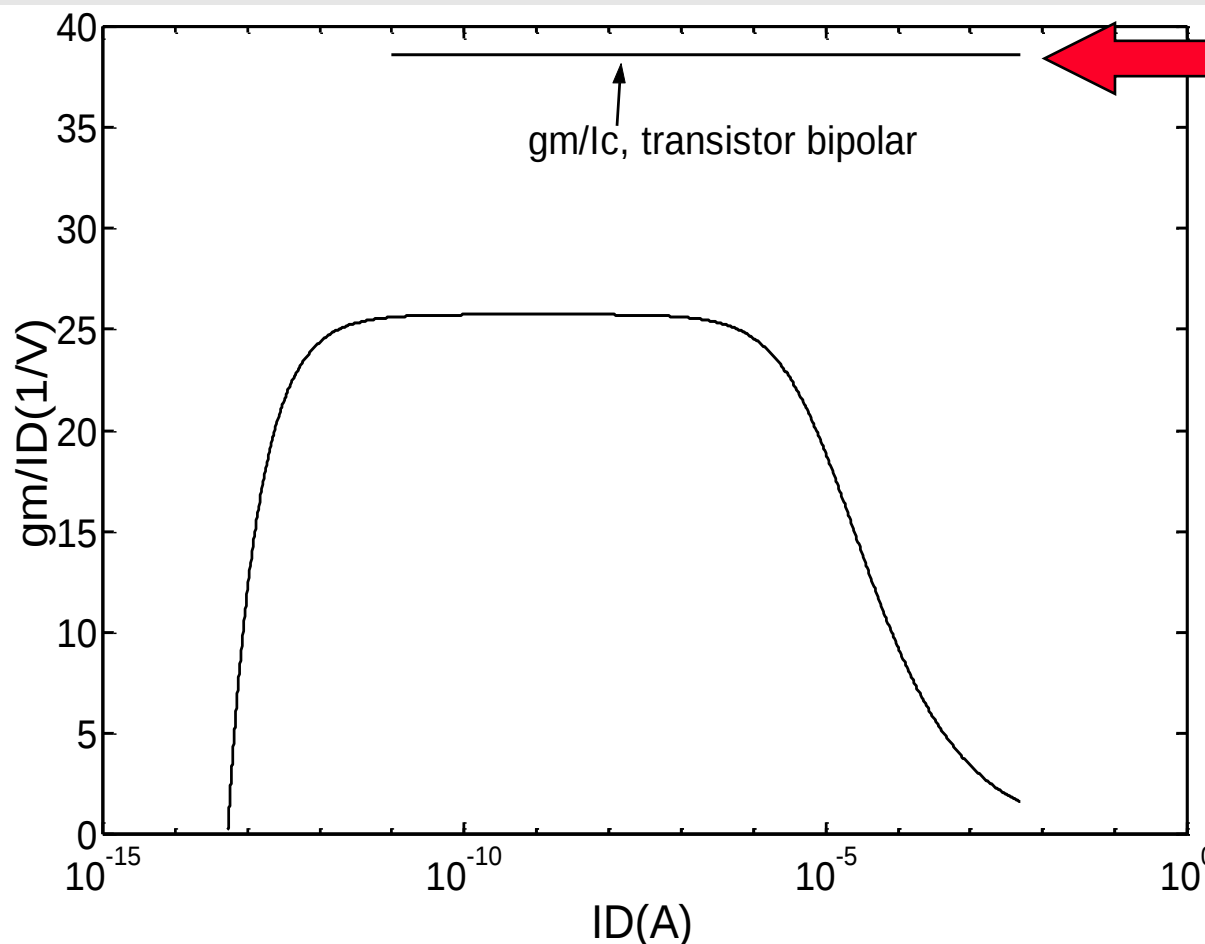

Bipolar Transistor:

$g_m/I_C$   
independent of  
current in a wide  
range


$W/L = 100$  and  
 $0.8\mu\text{m}$  technology.

- As the current increases, the “ $g_m$  generation efficiency decreases”
- To reach the maximum frequency allowed by the technology:  
 $\Rightarrow$  high  $g_m \Rightarrow$  high current  $\Rightarrow$  strong inversion  $\Rightarrow$  low efficiency
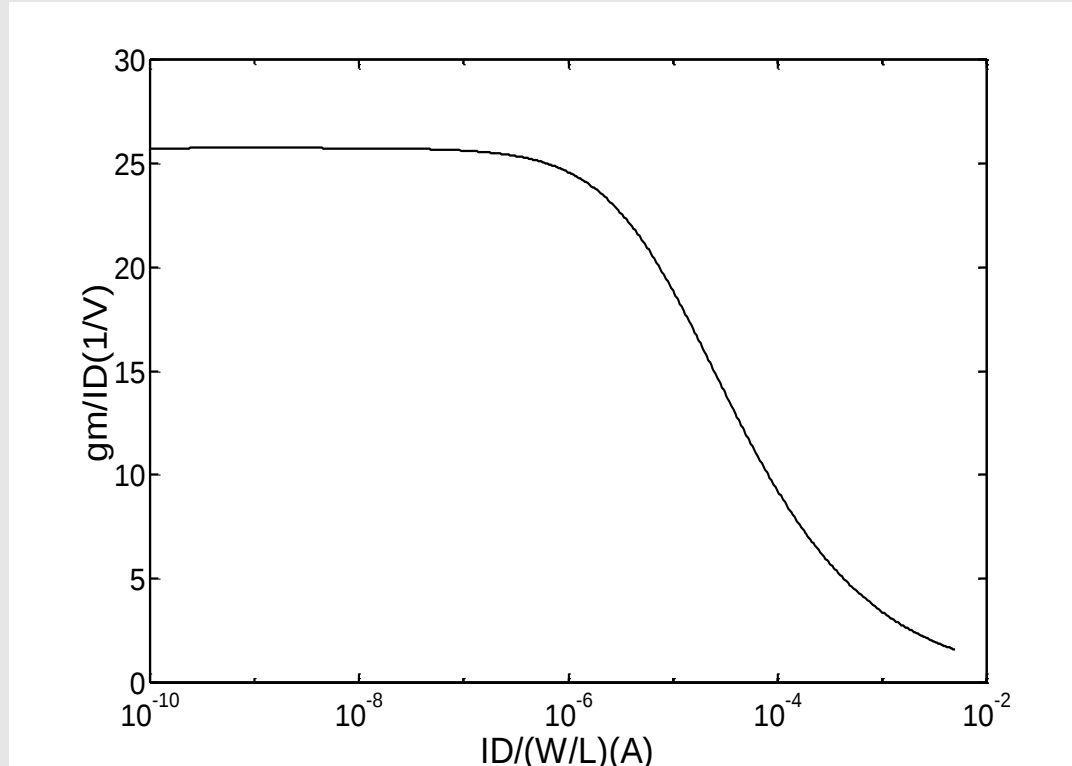
# $g_m/I_D$ and transistor size

When short channel effects are not significant:

$$I_D = \mu C_{ox} (W/L) \cdot f(V_G, V_S, V_D) \rightarrow \left( \frac{g_m}{I_D} \right) = f(I_{norm}) \quad I_{norm} = \frac{I_D}{(W/L)}$$



$$I_{norm} = \frac{I_D}{\mu C_{ox} (W/L)}$$


$$I_{norm} = i_f = \frac{I_D}{I_S}$$

When short channel effects are significant:


$$\left( \frac{g_m}{I_D} \right) = f(I_{norm}, L)$$
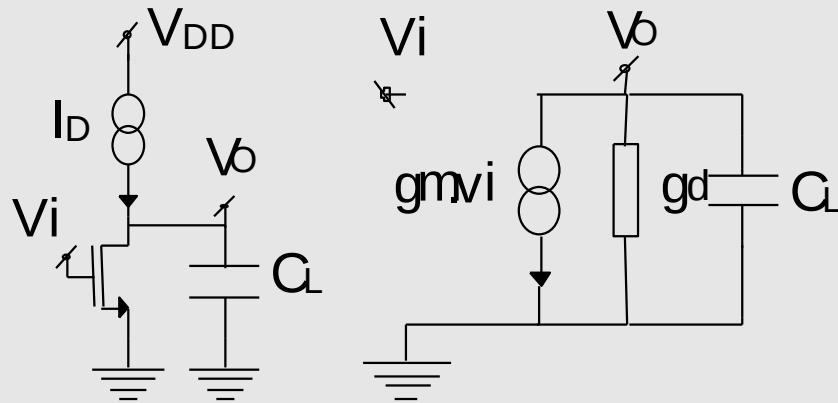
# Design Methodology: $g_m/I_D$ key variable

[Silveira, Flandre, Jespers, IEEE JSSC 1996, P.Jespers, Springer, 2010]


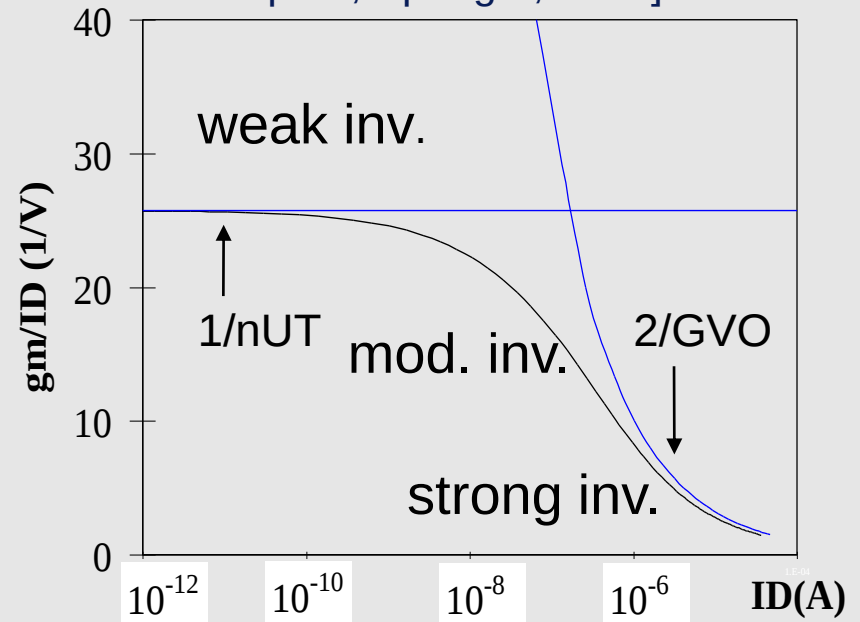
$$A_0 = \frac{g_m}{I_D} V_A \quad f_T = \frac{1}{2\pi} \frac{g_m}{C_L} = \frac{1}{2\pi C_L} \frac{g_m}{I_D} I_D$$




**Circuit Performance**

$$g_m / I_D$$

**Transistor Operating Mode**

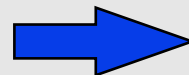**Transistor Sizing**


$$I_D = \mu C_{ox} (W/L) \cdot f(V_G, V_S, V_D)$$




$$\left( \frac{g_m}{I_D} \right) = f(I_{norm}) \quad I_{norm} = \frac{I_D}{(W / L)}$$

$$I_{norm} = \frac{I_D}{\mu C_{ox} (W / L)}$$

# Optimum of Power Consumption

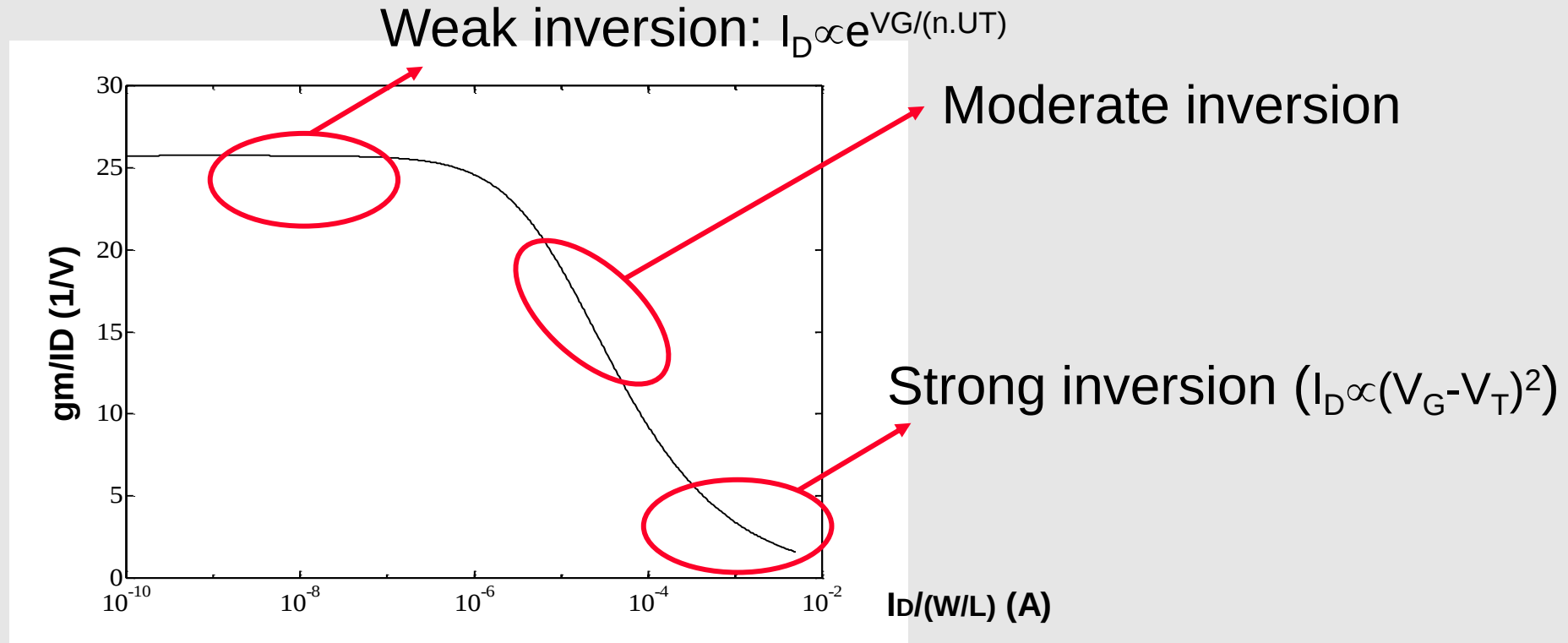


- Working towards WI

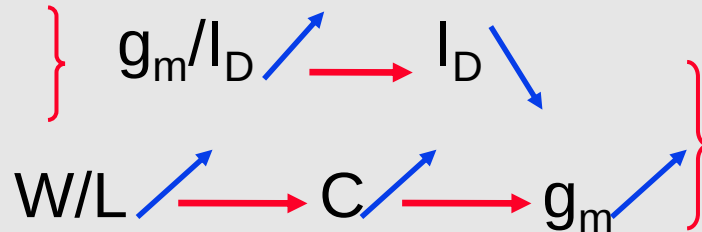




Usually an optimum exists in moderate inversion

# Example

## Intrinsic Amplifier: Power Optimum

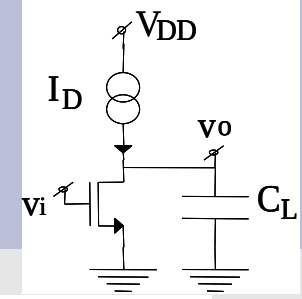


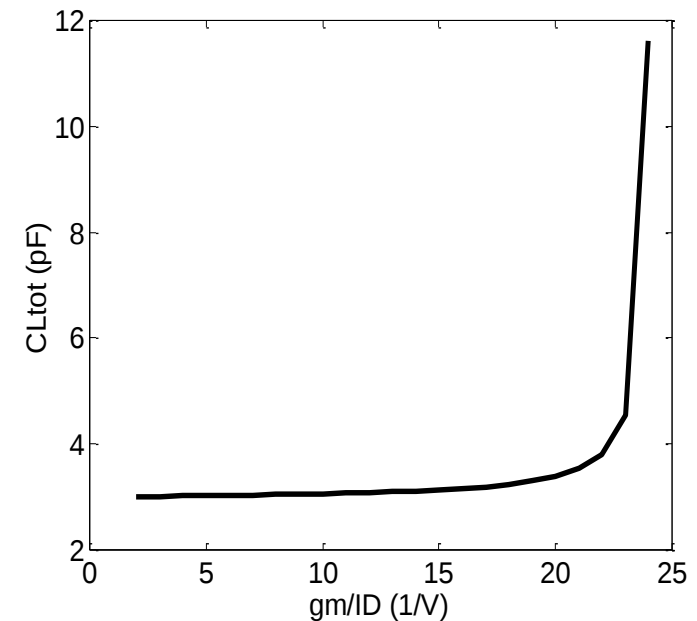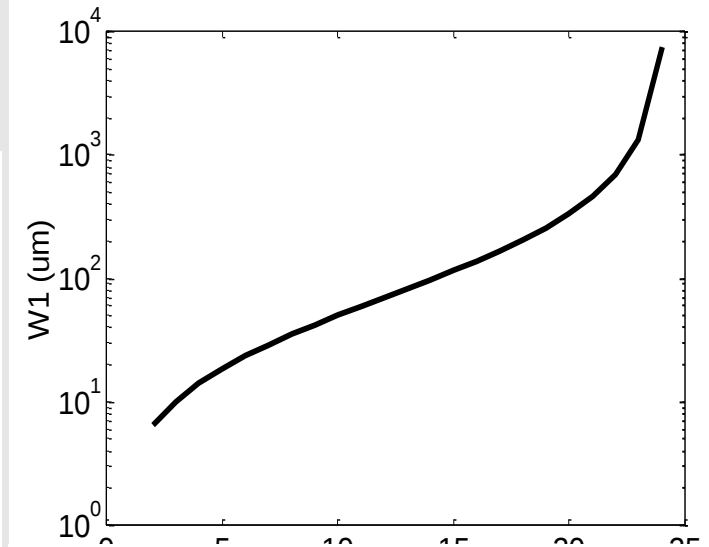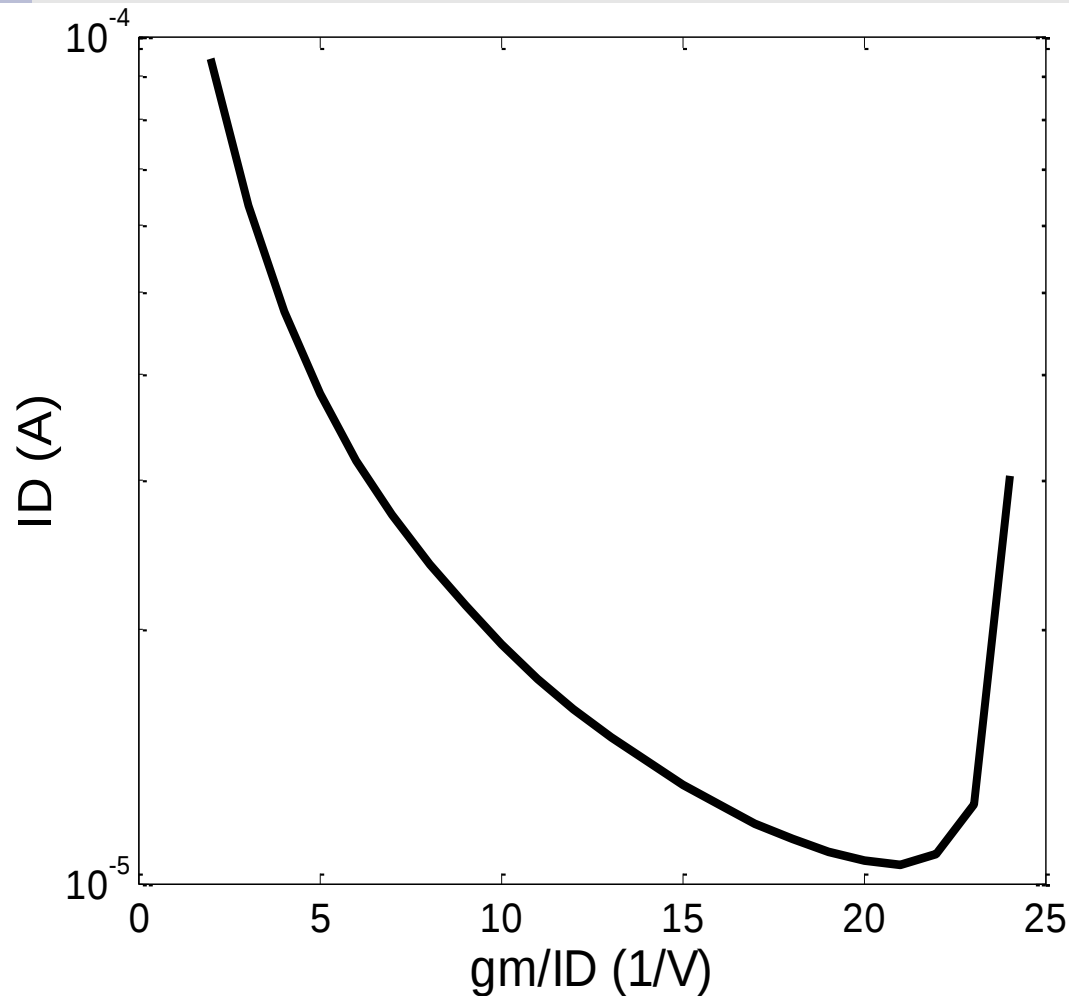$f_T=10\text{MHz}$ ,  $C_L=3\text{pF}$ ,  $L=2\mu\text{m}$ , tech:  $0.8\mu\text{m}$



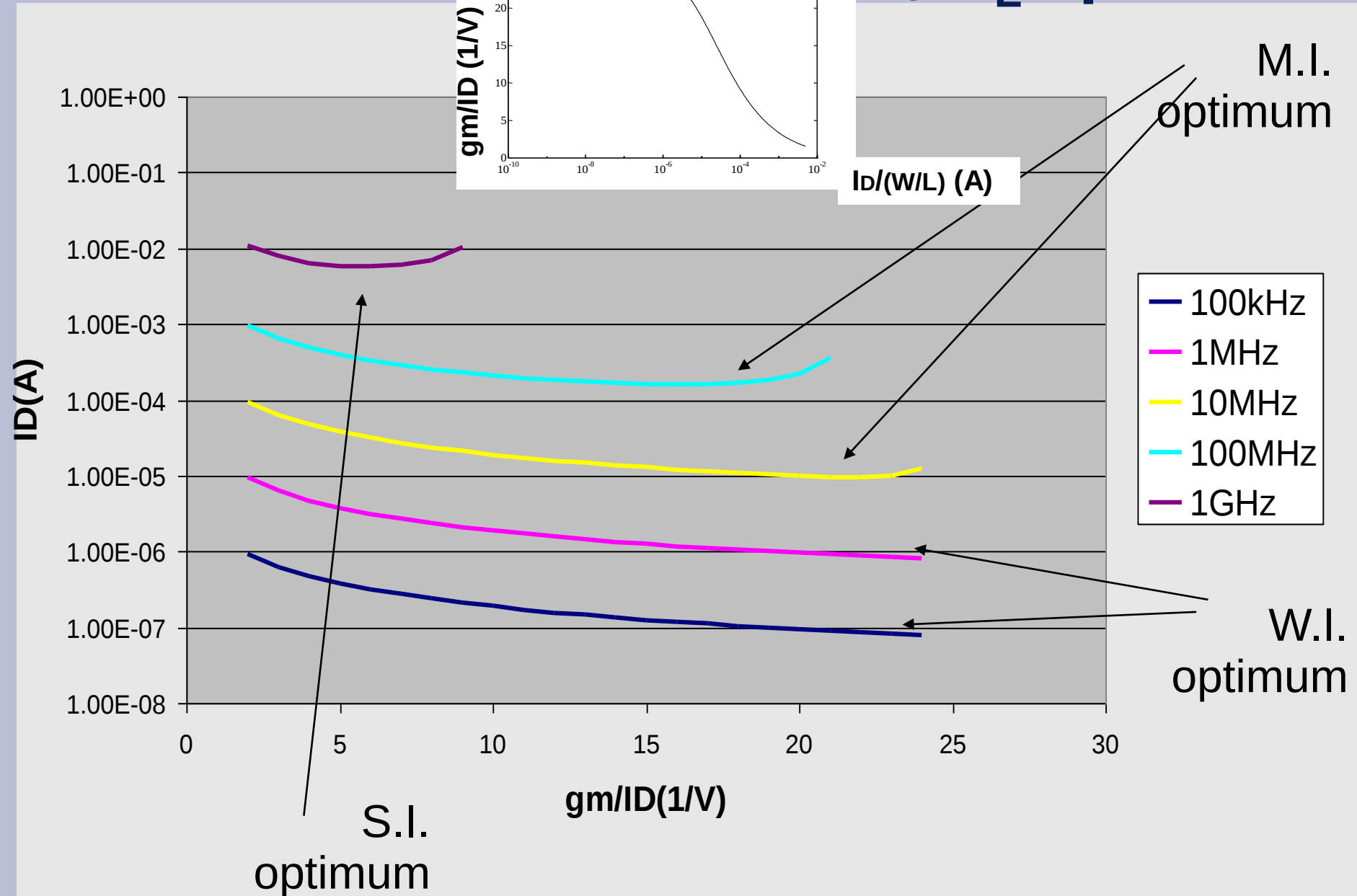
# Example

Intrinsic and extrinsic noise,  $C_L$  3pF




# gm/ID in the nanometer era

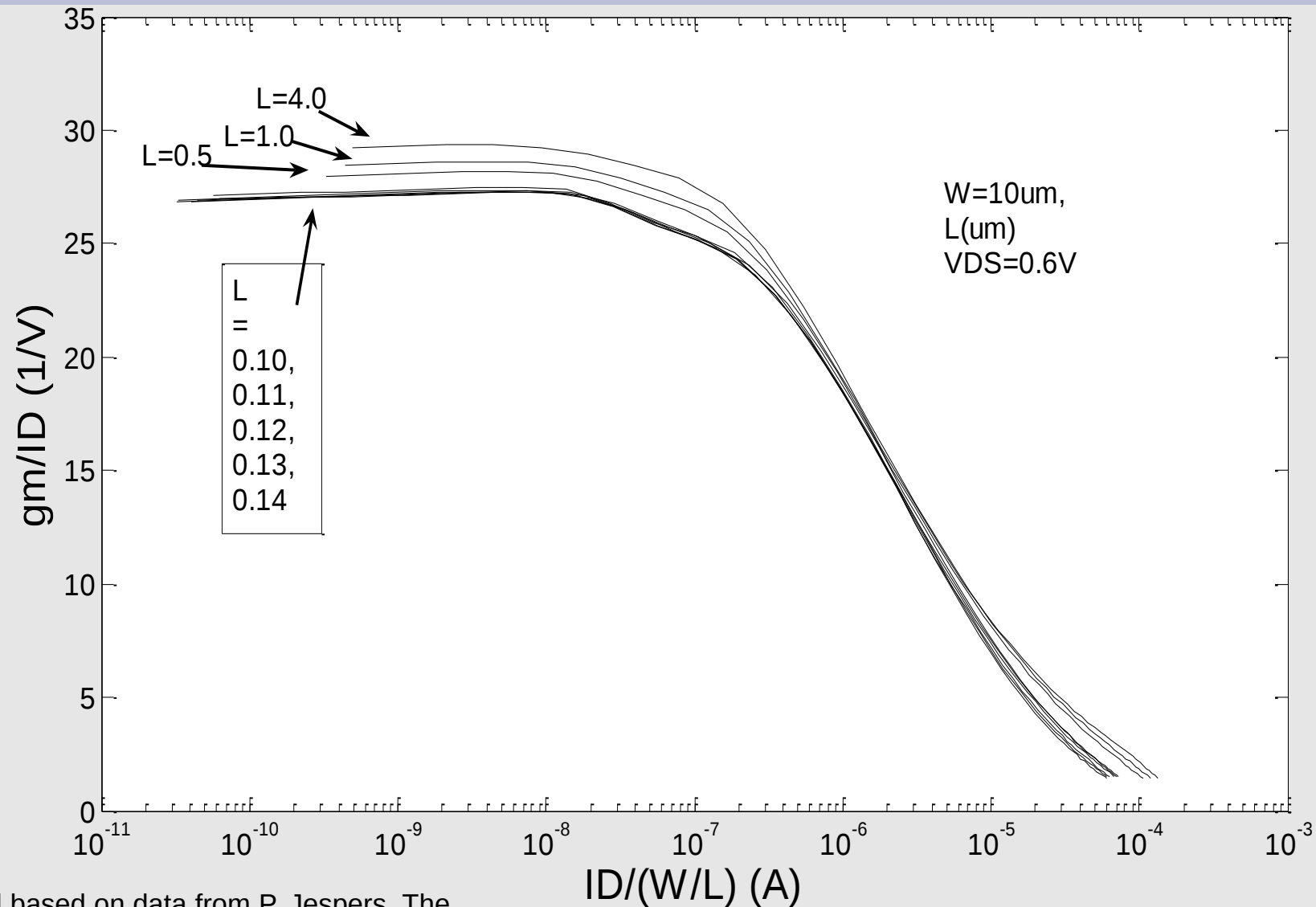



**Experimental data, 90nm CMOS process**

# gm/ID in the post CMOS era

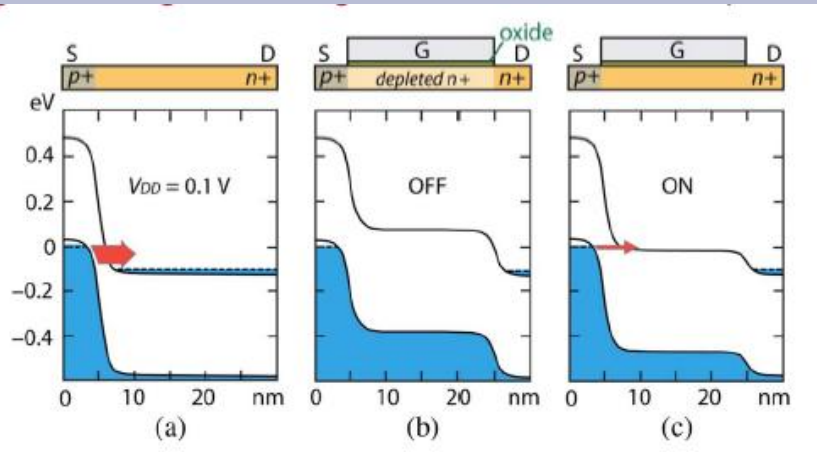

Seabaugh and Zhang: Low Voltage Tunnel Transistors for Beyond CMOS Logic

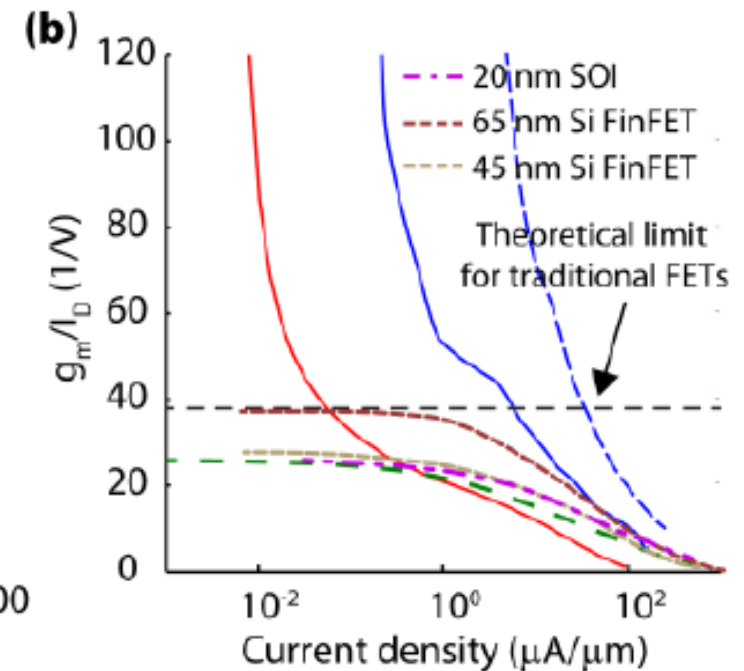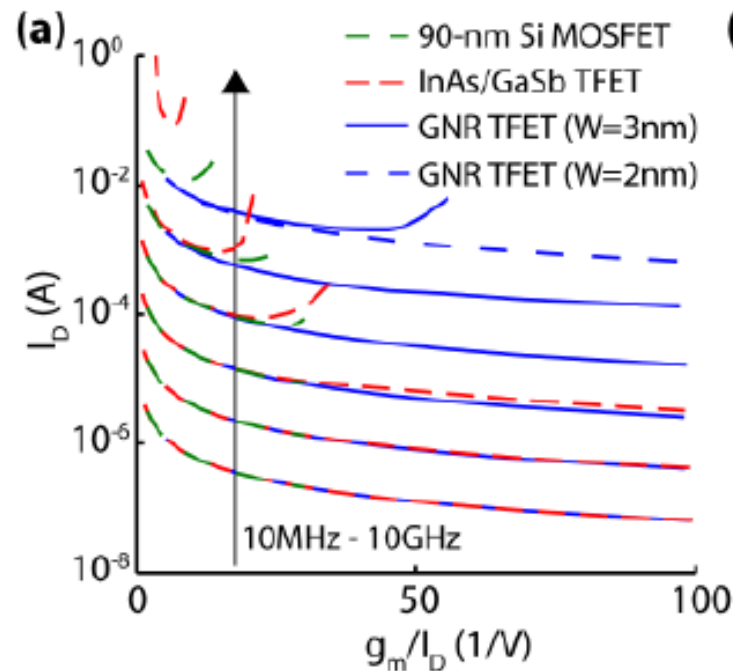B. Sensale-Rodriguez et al, IEEE SubVt 2012, joint work with U. Notre Dame, Indiana.




# Outline

- I. System: Active Implantable Medical Devices Today
- II. Transistors and Circuits: Analog Design for ULP.  
Transistor Modeling.  
Design Methodology.
- III. Circuit Techniques: Implementation of AIMDs blocks**
- IV. Conclusions and Prospects


# Example of modules: Pacemaker Activity Sense

## Objective:

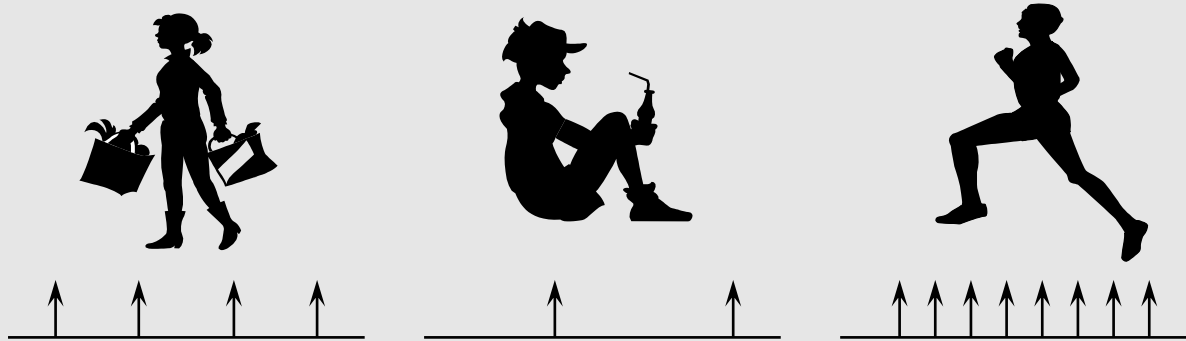


- ◆ E.g. Activity indicator: 3s Average of the absolute value of acceleration in the 0.5 - 7 Hz band.

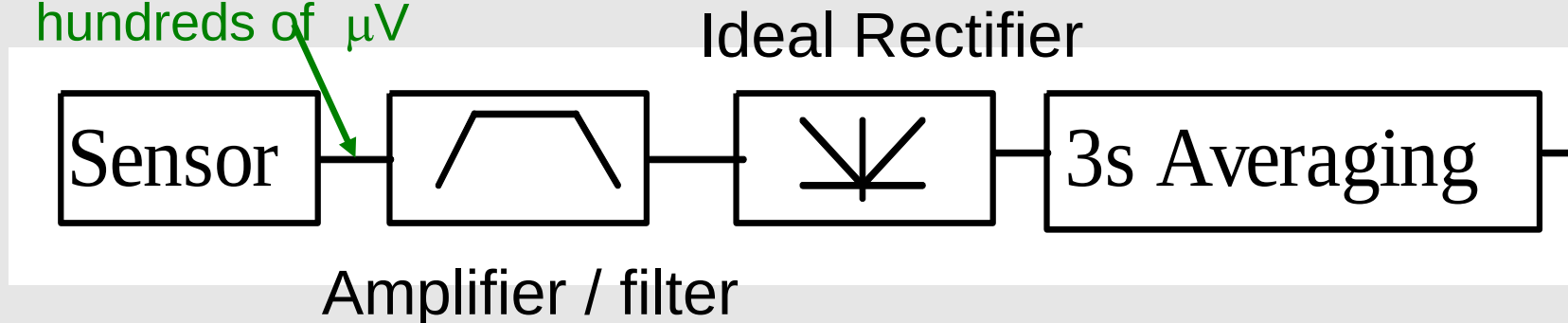Amplitude: tens to  
hundreds of  $\mu V$




# Accelerometer Signal Conditioning (1): Amplifier / Bandpass filter

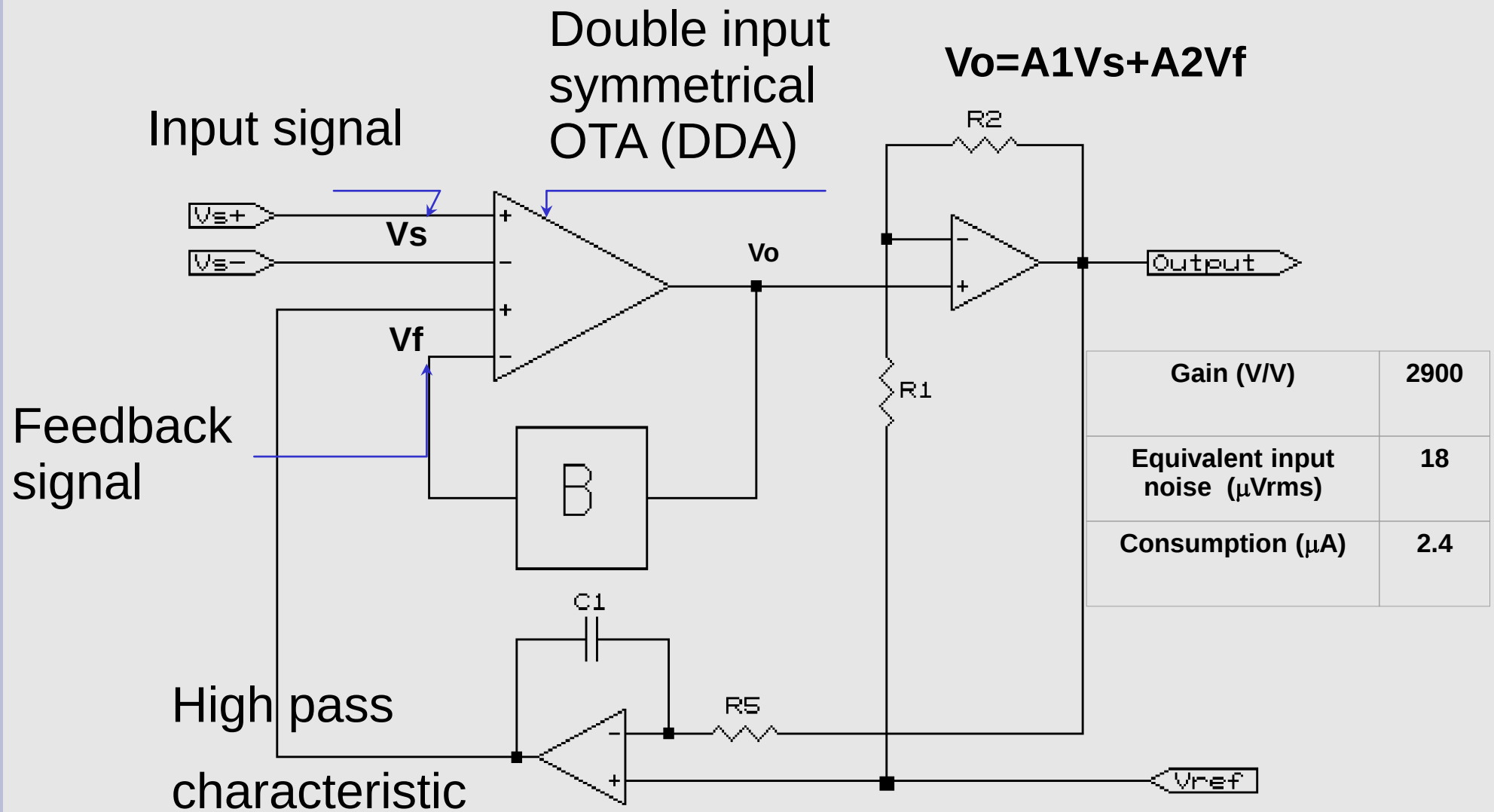

ISCAS 1998

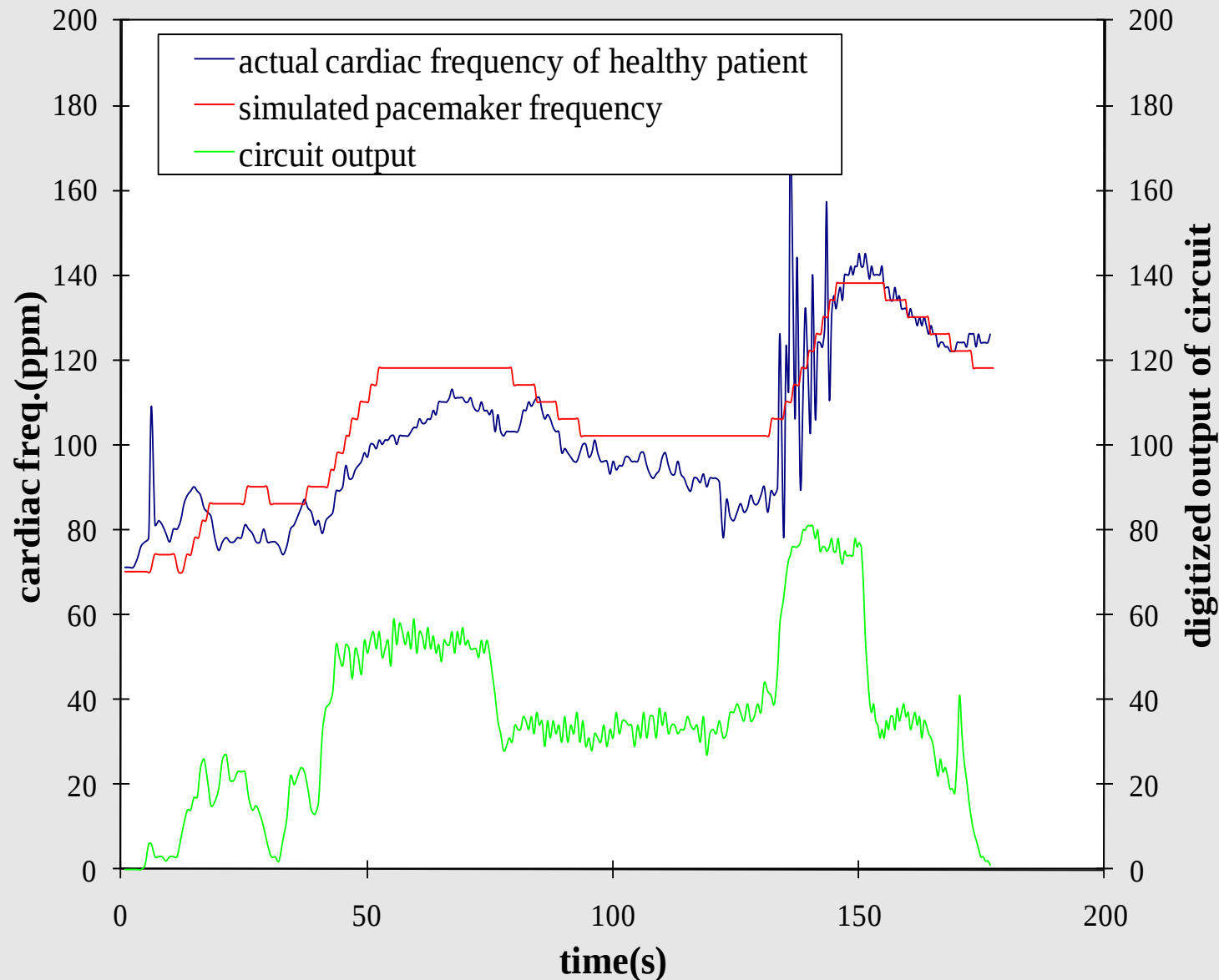
# Accelerometer Signal Conditioning (2): Results



# Accelerometer Signal Conditioning (3) : Gm-C implementation

A. Arnaud (UR), C. Galup (UFSC), ISCAS 2004

## Filtro-Amplificador 0.5-7Hz

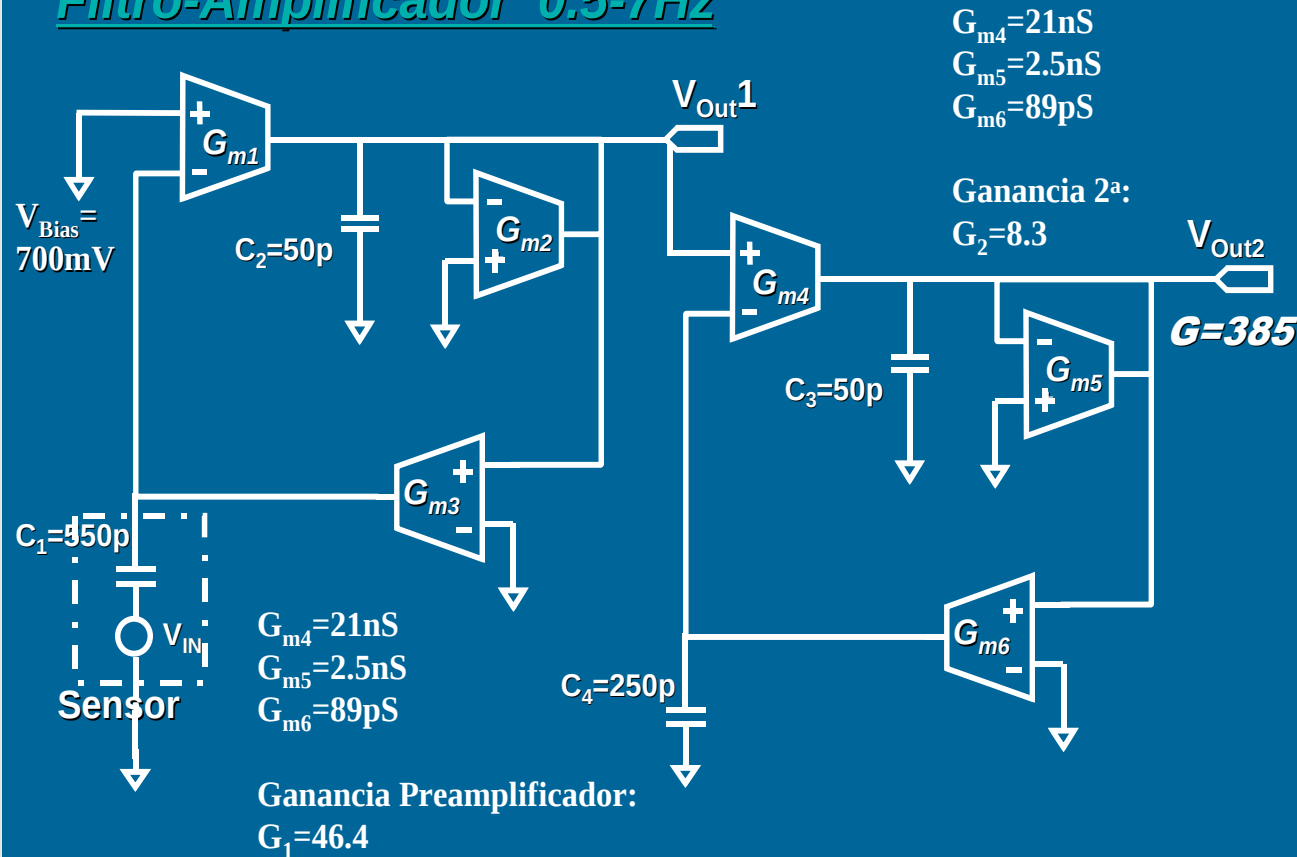

$I_{DD} = 290nA$



Equivalent  
Input noise:  
 $2.1\mu V_{rms}$

Gain: 390

Fully  
integrated
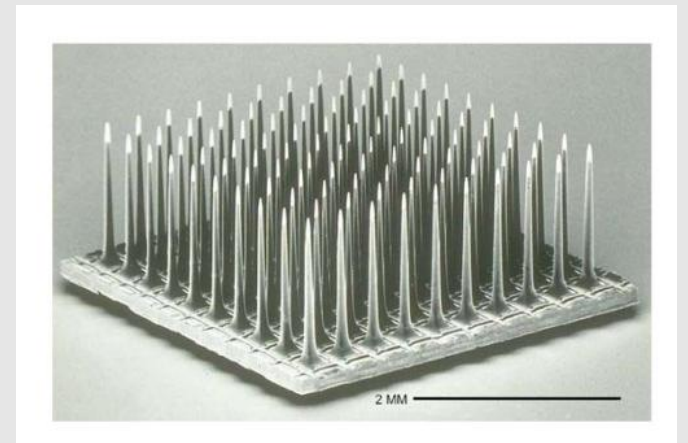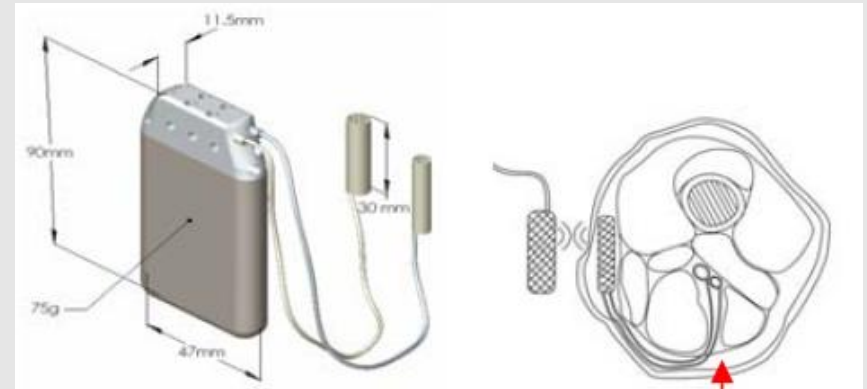
# Example of modules: Neural Recording Amplifier

- Objective: Signal detection from e.g: cuff electrodes or cortical electrodes arrays
- Requirements:
  - $0.5\mu\text{V}_{\text{rms}}$  -  $2\mu\text{V}_{\text{rms}}$  noise
  - BW: 300Hz – 8kHz
  - High CMRR (particularly in Cuff)
  - Block high DC offsets (100mV or more) due to electrode/tissue contact
  - Negligible DC input current
- A lot of research in this area ....




# Neural Amplifier Front End (1): Capacitive Feedback

- Inversion region for noise / power optimization: e.g. input pair weak inversion, current mirror active load: strong inversion
- CMRR limited by capacitor matching.

$$\text{NEF} = V_{ni, \text{rms}} \sqrt{\frac{2I_{\text{tot}}}{\pi \cdot U_T \cdot 4kT \cdot \text{BW}}}$$

|                        |                   |
|------------------------|-------------------|
| Gain                   | 40 dB             |
| BW                     | 0.13 Hz / 7.5 kHz |
| I <sub>total</sub>     | 16 μA             |
| NEF                    | 3.8               |
| v <sub>noise rms</sub> | 2.1 μV            |
| CMRR                   | > 42 dB           |


Harrison et al, IEEE JSSC, June 2003

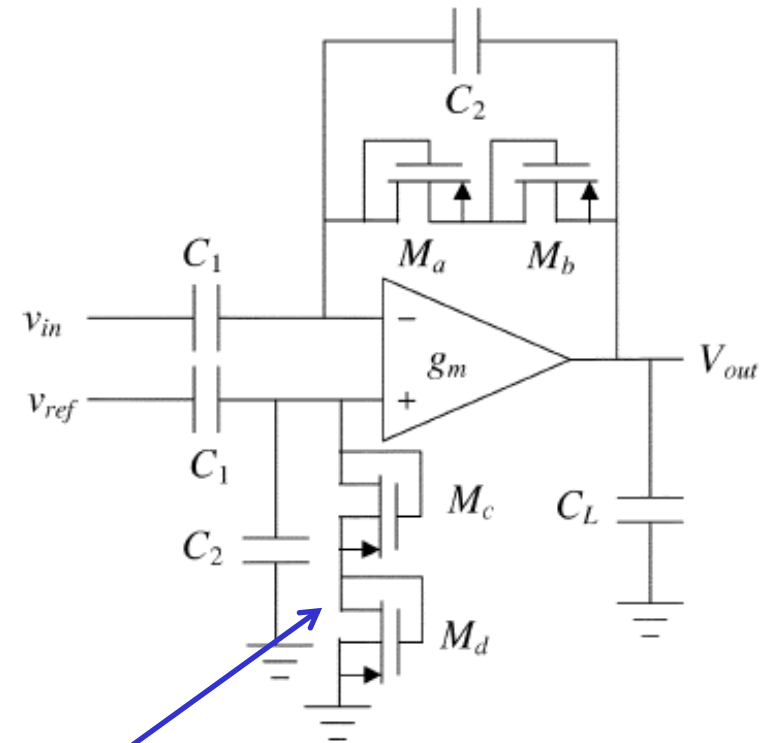

MOS –Bipolar Pseudoresistor (100s Mohms equivalent)
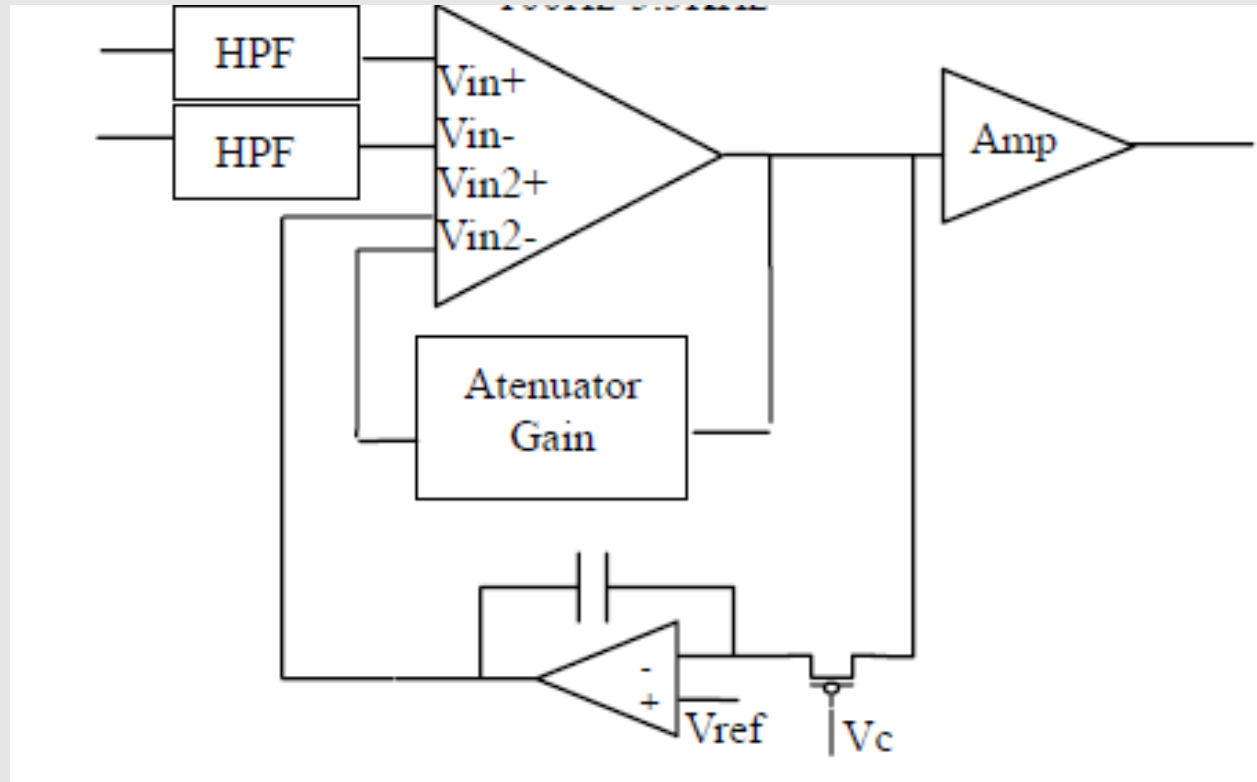
# Neural Amplifier Front End (2): DDA Based

- 😊 High CMRR  
(Given by Input Differential Pair)
- ☹️ Both Differential Pairs contribute equally to Input Noise (hence to area and consumption)




J. Sacristán, T. Oses, IFESS 2002,

Another DDA Based Scheme: M. Baru, U.S. Patent 6.996.435, 2006

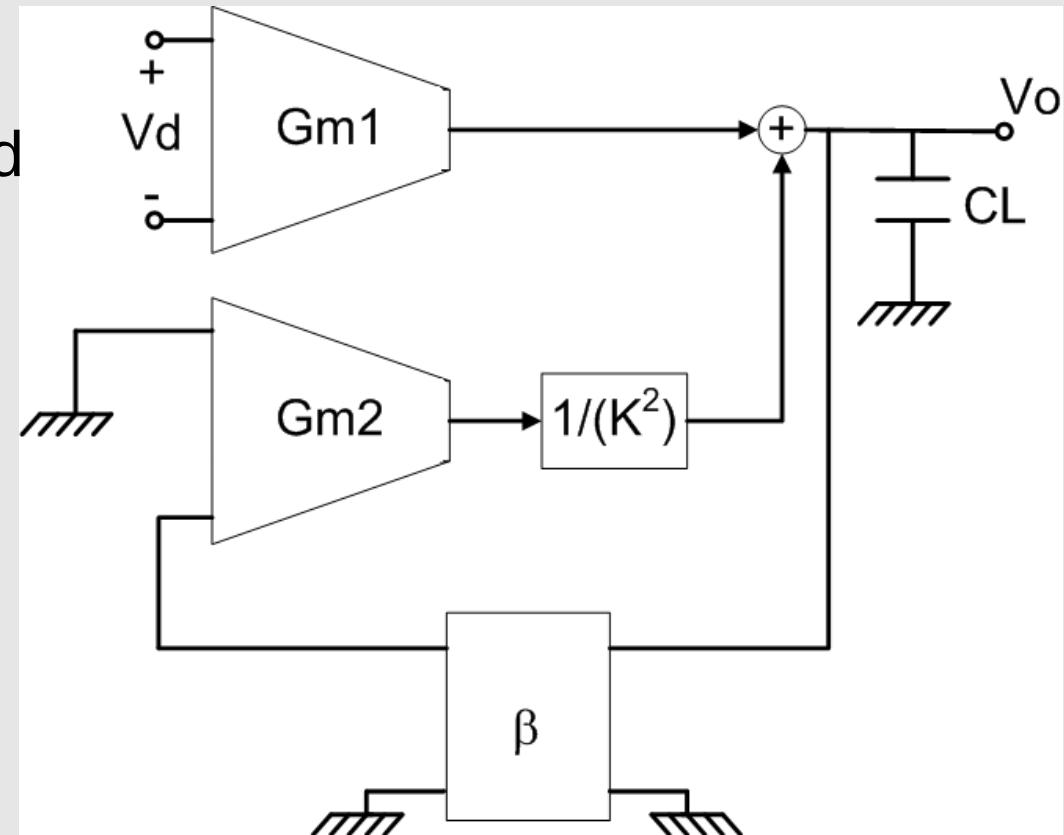
# Neural Amplifier Front End (3): “Asymmetrical” DDA Based (I)

P. Castro, F. Silveira, ISCAS 2011

- ☺ Effect of noise (and hence consumption and area) of Gm2 greatly reduced while keeping high CMRR (given by input differential pair)
- Gm2 less effective in compensating input offset and DC components => Output DC and high pass characteristic fixed by local feedback at the output


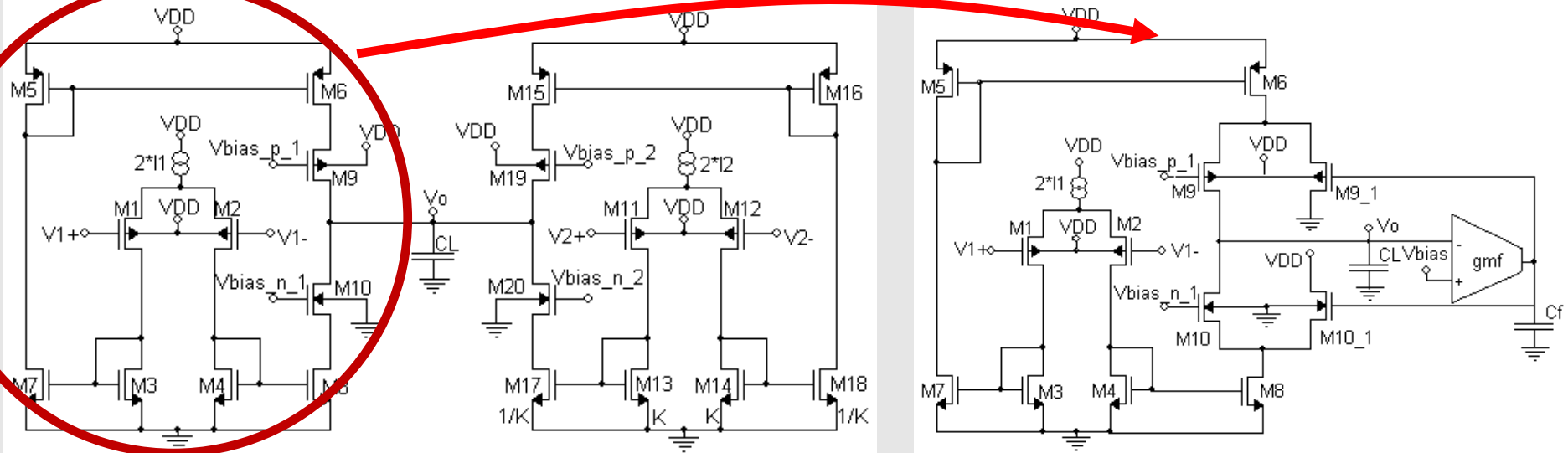
# Neural Amplifier Front End (4): “Asymmetrical” DDA Based (II)




| Spec                                               | Castro,<br>ISCAS 2011 | Harrison,<br>JSSC 2003 | Wattapanitch,<br>TR. BIOCAS<br>2007 | Sacristan,<br>IFESS 2002 |
|----------------------------------------------------|-----------------------|------------------------|-------------------------------------|--------------------------|
| Architecture                                       | Asym. DDA             | Capacitive             | Capacitive                          | DDA                      |
| A (dB)                                             | 48                    | 40                     | 41                                  | 80                       |
| NEF                                                | 4.2                   | 3.8                    | 2.7                                 | 53.4                     |
| I <sub>total</sub> ( $\mu$ A)                      | 16.5                  | 16.0                   | 2.7                                 | 180                      |
| v <sub>i</sub> noise<br>( $\mu$ V <sub>rms</sub> ) | 2.4                   | 2.1                    | 3.1                                 | 7.6                      |
| CMRR                                               | > 107                 | > 42                   | > 66                                | 90                       |

# Outline

- I. System: Active Implantable Medical Devices Today
- II. Transistors and Circuits: Analog Design for ULP.
  - Transistor Modeling.
  - Design Methodology.
- III. Circuit Techniques: Implementation of AIMDs blocks
- IV. Conclusions and Prospects**

# Prospects: Digital vs. Analog

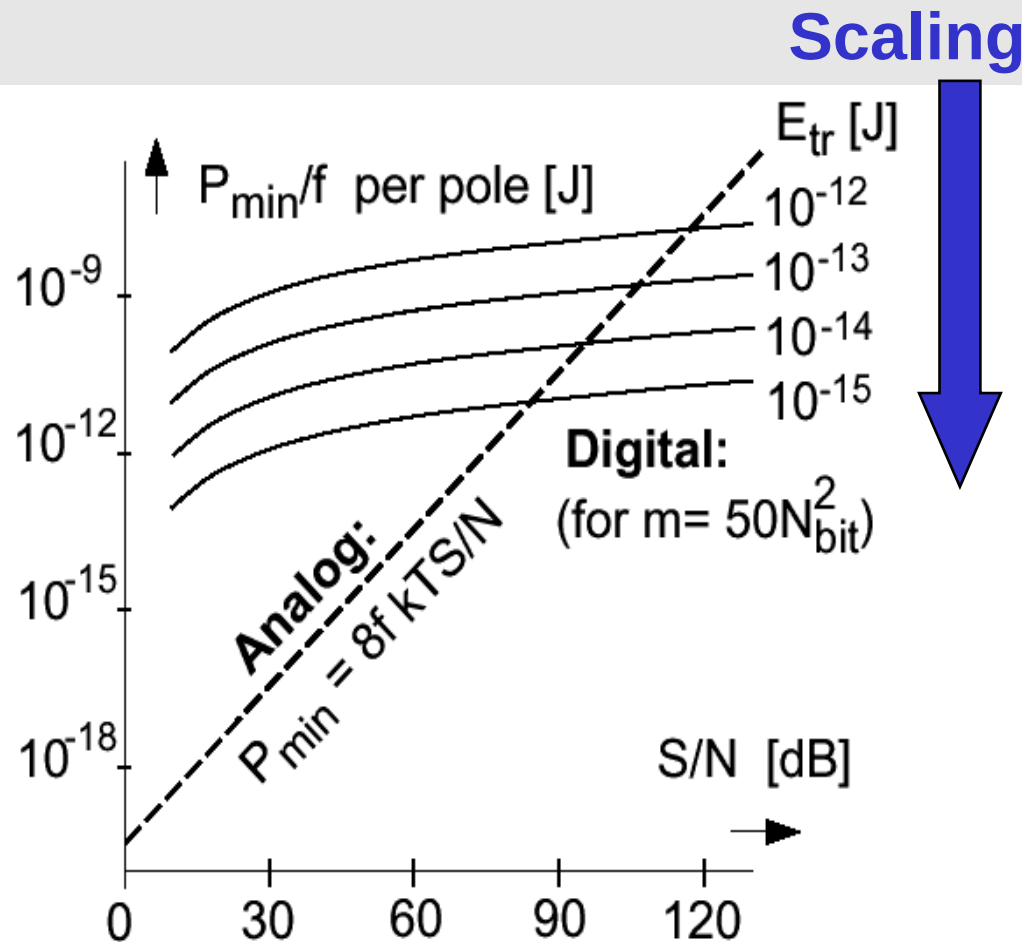

Source: E. Vittoz

- **Theoretical limits of power consumption for Analog and Digital Signal Processing**
- Analog better for low S/N, but the border is moving ...
- “Digital” pacemaker already present in marketing

# Prospects: Analog ULP and AIMD

- Intense growth of applications / therapies on development and reaching the market
- Broad Analog / Circuit research area:
  - Sensing
  - Stimulation, Power Management / Battery Recharge, Communication, ...
  - Once very specific area, now wider (wireless sensor networks, body area networks, portable devices, energy scavenging devices, RFID, ...).

# Prospects: AIMDs Brain Computer Interface

Set. 2000, Nicolelis, Duke University

BBC HOMEPAGE | WORLD SERVICE | EDUCATION low graph

**BBC NEWS**

You are in: **Sci/Tech**

Wednesday, 15 November, 2000, 19:37 GMT

## Monkey brain operates machine

Front Page

World

UK

UK Politics

Business

**Sci/Tech**

Health

Education


Entertainment

Talking Point

In Depth

AudioVideo

### Monkey robot brain

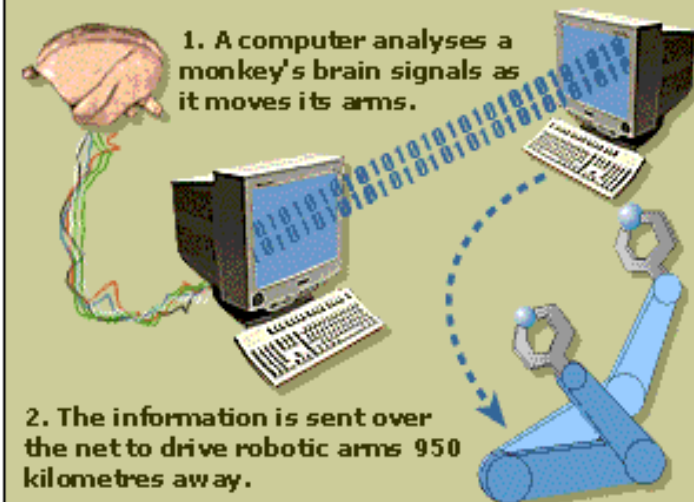

► **Miguel Nicolelis, Duke University**

"We are trying to investigate how could we tap into brain signals"

Scientists have used the brain signals from a monkey to drive a robotic arm.

As the animal stuck out its hand to pick up



# Prospects AIMDs: Brain Computer Interface

July 2004: Pilot FDA trial started by spin/off company of Brown Univ., several tetraplegic patients implanted.



# Some Conclusions

- ULP ICs for AIMDs: Each nA counts => **Methodology and Optimization**
- AIMDs: Very broad field in strong expansion
  - ✓ Many R & D opportunities
  - ✓ Microtechnology is often the enabling factor.
- AIMDs: Price is not the main concern, but application and performance
  - ✓ Suitable for developments with lower volume productions than in other areas
  - ✗ High investment associated with long development cycles, qualification, clinical testing and regulatory aspects.

# Microelectronics Group – IIE Universidad de la República

More Information

[iie.fing.edu.uy/vlsi](http://iie.fing.edu.uy/vlsi)

[silveira@fing.edu.uy](mailto:silveira@fing.edu.uy)



## Acknowledgements

- CCC Medical Devices, NanoWattICs
- Members (present and past) of Microelectronics Group, UR

# Upcoming Regional Events

## LASCAS 2014

5<sup>th</sup> IEEE Latin American Symposium on Circuits and Systems  
Santiago, Chile  
February 25-28, 2014

*Iberchip*  
XX workshop



Deadline: 1<sup>st</sup> Nov, 2013

10<sup>th</sup> Nov, 2013

2014 IEEE  
International Instrumentation  
and Measurement Technology  
Conference  
May 12-15, 2014 - Montevideo, Uruguay

Deadline: 15<sup>th</sup> Oct, 2013

## LASCAS / Iberchip 2015: Uruguay

Thank you !