

RLC series circuit made simple and portable with smartphones

Ives Torriente-García¹, Arturo C. Martí², Martín Monteiro³, Cecilia Stari², Juan C. Castro-Palacio¹, Juan A. Monsoriu¹

¹Centro de Tecnologías Físicas, Universitat Politècnica de València, 46022 València, Spain

²Instituto de Física, Universidad de la República, 11400 Montevideo, Uruguay

³Universidad ORT Uruguay, 11100 Montevideo, Uruguay

Abstract

This article presents a novel method for studying RLC series circuits using two smartphones, one used as a signal generator and the other as an oscilloscope. We measure the voltage at the external resistor as a function of frequency when subjected to a sinusoidal electromotive force. The experimental results demonstrate a remarkable agreement with the theoretical curve for the voltage at the resistor and the resonance frequency, validating the accuracy of the smartphone-based setup. The experiment fills the gap in educational materials related to electrical circuits and provides a portable alternative to traditional, expensive laboratory equipment.

Introduction

Physics experiments using smartphone sensors are very common to see nowadays for both secondary and introductory Physics courses at the university level.¹ These experiments are proven to foster the motivation and independence of students what positively impacts their academic performance. However, in this broad range of works some topics are more represented than others, for instance, mechanics,^{2,3} oscillations,⁴ beats,⁵ acoustics,⁶ and optics.⁷ The published work on electromagnetism using smartphone sensors involves mostly the measurement of magnetic fields.⁸⁻¹⁰ However, experiments relating electrical circuits appear in a much lesser extent.^{11,12}

Direct and alternating current circuits combining resistors, capacitors and coils such as RC, RL, and RLC series circuits are commonly seen in secondary and introductory physics courses.¹²⁻²⁰ Most published work on simple circuits includes the study of charge and discharge of a capacitor in an RC series circuit,^{12,14} and current variations upon connecting and disconnecting an RL series circuit.^{15,16} With regard to RLC circuits,¹⁷⁻²⁰ we would like to point out a very simple work²⁰ where the resonance curve (voltage at the capacitor versus the frequency) was obtained using a voltmeter instead of an oscilloscope. We go beyond in this work and substitute the signal generator and the oscilloscope by smartphones. This idea was first proposed in reference.¹² In this article, authors used the headphone port designed for connecting an external microphone and speakers to read data from an external circuit. On the other hand, in reference²¹ authors proposed to transform a smartphone in an arbitrary signal generator by means of using a java code for Android. Here we make it simple by using the *Tone Generator* option available in the free app for Android Physics Sensors Toolbox Suite.²² Another way of turning a smartphone into an oscilloscope takes the advantage of Arduino boards to communicate with a smartphone using the bluetooth interface,²³ which is a valuable option for smartphones not including a headphone port.

In this paper we present a simple method to study an RLC series circuit connected to a sinusoidal electromotive force. To achieve simplicity and portability, we utilized two smartphones, one as a signal generator and the other as an oscilloscope, replacing the

expensive equipment commonly found in physics laboratories. By employing smartphones, we have not only reduced the cost of the experiment but also made it accessible outside the confines of the physics laboratory, providing students with the opportunity to conduct the study in various settings.

The experiment

Figure 1 shows the experimental setup used in this study. A picture of the actual setup is shown on the left-hand side, and a schematic representation of the circuit is shown on the right-hand side. A Samsung Galaxy S52 smartphone was used as the signal generator and another, a smartphone Redmi Note 7, is used as the oscilloscope. The RLC circuit is formed by a resistor of resistance $R=(220.0\pm 4.4\ \Omega)$ (manufacturer value), an inductor or coil of inductance $L=(10.37\pm 0.25)$ mH (measured with a digital LRC meter, model PROSTER BM4070) and a capacitor of capacitance $C=(1.00\pm 0.01)$ μF (manufacturer value). The internal resistance of the smartphone used as signal generator was $R_i=(10.620\pm 0.002)\ \Omega$ when measured with a fixed multimeter Keysight 34461A. The ohmic resistance of the coil, $R_L=(19.381\pm 0.003)\ \Omega$, was also measured with the same equipment. $R_T=R+R_i+R_L=(250.0\pm 4.4)\ \Omega$ is the total ohmic resistance of the circuit. The maximum voltage at the resistor which is directly proportional to the maximum current (see Eq. 3 below) was measured with another smartphone used as oscilloscope.

The signal generation capability is achieved using the *Tone Generator* included in the free Android app Physics Sensors Toolbox Suite.²² The *Tone Generator* can be found on the left panel of the main screen of the app. The frequency (0 - 20000 Hz) and type of signal (sinusoidal, square, saw-tooth, triangular) are the parameters available to set up. The amplitude of the generated wave can be controlled by changing the volume of the phone. An audio jack has been used to allow the signal out. On the other hand, the second smartphone was used as oscilloscope by means of the option *Audio Scope* included in the free Android app phyphox.²⁴ This option visualizes any audio sent in using the jack connector, which means in this paper the voltage at the external resistor. We should point out that not all smartphones perform well as oscilloscopes therefore we recommend to first check that the measured signal is not deformed. The free app(s) used in this work can be seen on the screenshots shown in Fig. 1. The picture was taken while the app(s) were being used.

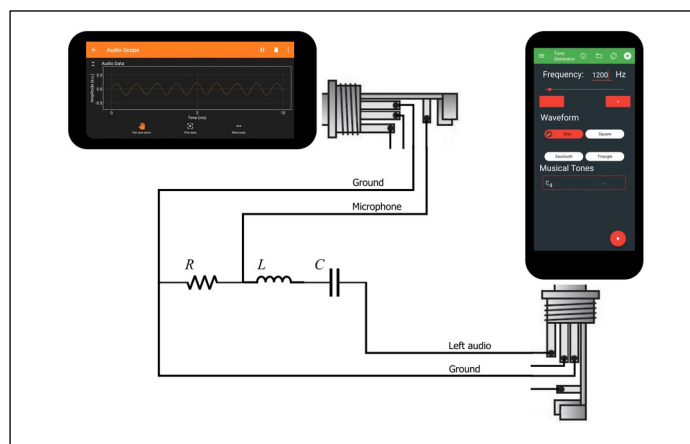


Fig. 1. Schematic representation of the experimental setup. The free app(s) used in this work can be seen on the screens of the smartphones.

Results

First, we have studied the range of voltages at the audio port when a sinusoidal wave is generated with Physics Sensors Toolbox Suite²³. For this purpose, we have used a conventional oscilloscope (model Tektronix TBS 1072B-EDU) to measure the amplitude of the electromotive force (ε_{max}) for each step of the volume button of the smartphone. Figure 2 shows the values of ε_{max} as a function of the number of steps of the volume button (a total of $n = 15$ steps). The measures of ε_{max} have been taken for a low (250 Hz) and high value (12 kHz) of frequency within the range used in this work (0 - 12 kHz) and results are largely the same (Figure 2). For all measurements, the volume has been set at step $n = 7$ (out of 15 steps available) which corresponds to 32.4 mV. Keeping the volume step at $n = 7$, we also measured the voltage with phyphox app to obtain 0.516 a.u. (arbitrary units). It means that the a.u. to volt conversion is 0.062 V/a.u.

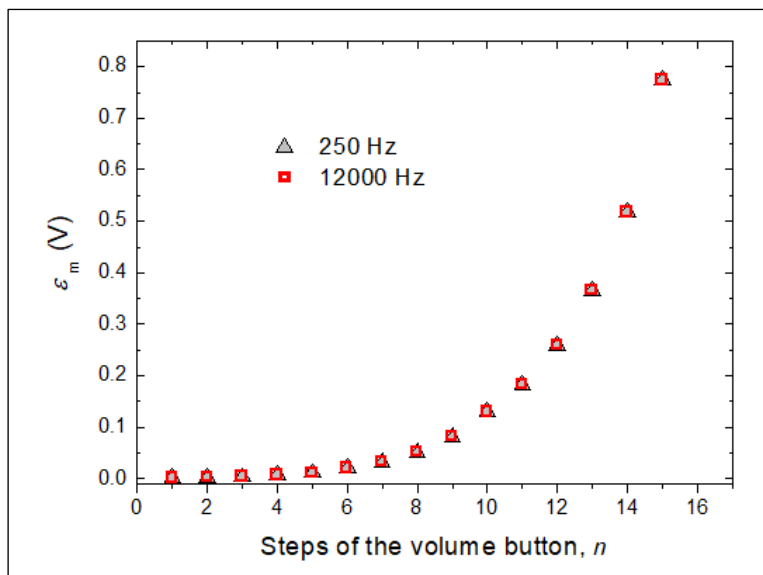


Fig. 2. Maximum electromotive force at the audio port of the smartphone (ε_{max}) as a function of the number of steps of the volume button. The values have been measured using a conventional oscilloscope (model Tektronix TBS 1072B-EDU)

An important phenomenon when it comes to the study of RLC series circuits is resonance. It is given when the capacitive reactance (X_C) and the inductive reactance (X_L) are equal. Then, the general impedance becomes a real number which is equal to the ohmic resistance of the circuit $Z = R_T$. For the resonance frequency the maximum current is maximal, $I_m = \varepsilon_m / R_T$. We can know about the behaviour of the current by looking at the voltage at the resistor as these two quantities are directly proportional (Eq. 3).

Table 1 registers the values of the maximum voltage at the resistor (V_{Rm}) measured with the smartphone used as oscilloscope as a function of the frequency (f) of a sinusoidal wave used as input and originated at the smartphone used as signal generator. These values are shown in Fig. 2.

Table I. Values of the maximum voltage at the resistor (V_{Rm}) as a function of the frequency (f) of the sinusoidal wave used as input in the RLC series circuit.

f (Hz)	V_{Rm} (a.u.)	f (Hz)	V_{Rm} (a.u.)	f (Hz)	V_{Rm} (a.u.)
100	0.0540	1650	0.4387	5000	0.2726
200	0.1260	1700	0.4372	5500	0.2559
300	0.1820	1750	0.4374	6000	0.2370
400	0.2323	1800	0.4395	6500	0.2207
500	0.2750	2000	0.4317	7000	0.2030
600	0.3162	2200	0.4199	7500	0.1968
700	0.344	2400	0.4072	8000	0.1864
800	0.3676	2600	0.3958	8500	0.1785
900	0.3845	2800	0.3875	9000	0.1706
1000	0.4048	3000	0.3796	9500	0.1595
1100	0.4182	3200	0.3612	10000	0.1550
1200	0.4243	3400	0.3532	10500	0.1470
1300	0.4315	3600	0.3416	11000	0.1324
1400	0.4378	3800	0.3307	11500	0.1294
1500	0.4405	4000	0.3155	12000	0.1246
1600	0.4410	4500	0.2958		

The maximum current established at the RLC series circuit when it is powered with a sinusoidal electromotive force (ε) is calculated as:

$$I_m = \frac{\varepsilon_m}{|Z|}, \quad (1)$$

where ε_m is the maximum electromotive force and $|Z|$ is the modulus of the complex impedance. By substituting the expression for the modulus of the impedance the above equation becomes:

$$I_m = \frac{\varepsilon_m}{\sqrt{R_T^2 + (X_L - X_C)^2}} = \frac{\varepsilon_m}{\sqrt{R_T^2 + (2\pi fL - 1/(2\pi fC))^2}}, \quad (2)$$

Where L is the inductance of the coil, C the capacitance of the capacitor, and $R_T = R + R_i + R_L$ is the total ohmic resistance. As mentioned above, the terms R , R_i and R_L represent the resistance of the external resistor, the internal resistance of the smartphone used as generator and the ohmic resistance of the inductor, respectively. The maximum voltage at the resistor which depends on the frequency can be represented as:

$$V_{Rm}(f) = I_m R = \frac{\varepsilon_m R}{\sqrt{R_T^2 + (2\pi fL - 1/(2\pi fC))^2}} \quad (3)$$

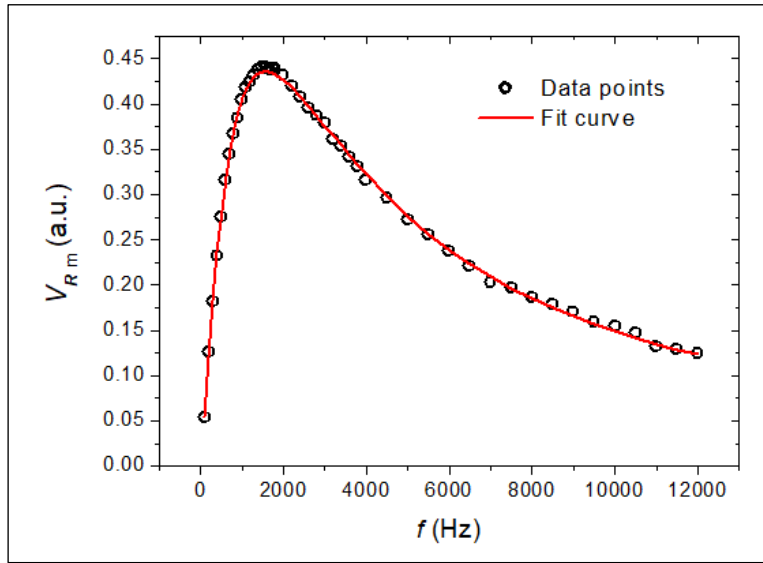


Fig. 3. Maximum voltage at the resistor (V_{Rm}) as a function of the frequency (f). The data points (open circles) are shown along with the fitting curve using the theoretical expression (red solid line).

In order to test the suitability of the experimental setup to study the RLC series circuit, the expression of $V_{Rm}(f)$ in Eq. (3) has been fitted to the experimental data (red solid line in Figure 2). Two parameters have been left free, namely, the maximum electromotive force (ε_m) and the resonance frequency (f_0). The resulting fitted value for the maximum is $V_{Rm} = (0.452 \pm 0.003)$ a.u., and for the resonance frequency $f_0 = (1560.5 \pm 5.9)$ Hz. The overall quality of the fitting is good with a correlation coefficient of 0.999. By using the fitted resonance frequency and the value reported by the manufacturer for the capacitance, the inductance of the coil can be calculated from eq. 3 as $L = (1/C) [1/(2\pi f_0)]^2 = (10.4 \pm 0.1)$ mH which compares very well to the previously measured value $L = (10.37 \pm 0.25)$ mH. On the other hand, using the fitted maximum electromotive force and the value reported by the manufacturer for the resistance, the total ohmic resistance of the circuit can be calculated from eq. 3 at resonance, $R_T = R \frac{\varepsilon_m}{V_{Rm}} = (251 \pm 8) \Omega$, which compares very well to the total ohmic resistance of the circuit previously mentioned, $R_T = (250.0 \pm 4.4) \Omega$.

Finally, it should be pointed out that for values of frequency beyond 12000 Hz the sinusoidal signal started to look distorted on the screen of the smartphone used as oscilloscope.

Final remarks

Two smartphones, one used as a signal generator, and another as an oscilloscope are good enough to carry out a quantitative study of the frequency curve in the RLC series circuit when it is connected to a sinusoidal electromotive force. The theoretical curve for the voltage at the

resistor as a function of the frequency agrees very well with the experimental data. Similarly, the theoretical resonance frequency agrees well with the measured one. These results indicate the suitability of the smartphones for this type of AC current experiment. The low cost and portable experiment presented in this work can be easily implemented as a laboratory in secondary and first year physics courses contributing in this way to increase the motivation, independence, and academic performance of the students.

References

- [1] M. Monteiro and A.C. Martí, "Resource letter MDS-1: Mobile devices and sensors for physics teaching," *Am. J. Phys.* 90, 328–343 (2022).
- [2] P. Vogt and J. Kuhn, "Experiments using cell phones in physics classroom education: The computer-aided g determination," *Phys. Teach.* 49, 383–384 (2011).
- [3] I. Salinas, M. Monteiro, A. C. Martí, and J. A. Monsoriu, "Analyzing the dynamics of a yo-yo using a smartphone gyroscope sensor," *Phys. Teach.* 58, 569–571 (2020).
- [4] J. C. Castro-Palacio, L. Velazquez-Abad, M. H. Gimenez, and J. A. Monsoriu, "Using a mobile phone acceleration sensor in physics experiments on free and damped harmonic oscillations," *Am. J. Phys.* 81, 472–475 (2013).
- [5] M. H. Giménez, J. C. Castro-Palacio, and J. A. Monsoriu, "Direct visualization of mechanical beats by means of an oscillating smartphone," *Phys. Teach.* 55, 424–425 (2017).
- [6] J. A. Gómez-Tejedor, J. A. Castro-Palacio and J. A. Monsoriu, "The acoustic Doppler effect applied to the study of linear motions," *Eur. J. Phys.* 35, 025006 (2014).
- [7] I. Salinas, M. H. Giménez, J. A. Monsoriu and J. C. Castro-Palacio, "Characterization of linear light sources with the smartphone's ambient light sensor," *Phys. Teach.* 56, 562–3 (2018).
- [8] E. Arribas, I. Escobar, C. P. Suarez, A. Najera, and A. Beléndez, "Measurement of the magnetic field of small magnets with a smartphone: a very economical laboratory practice for introductory physics courses," *Eur. J. Phys.* 36, 065002 (2015).
- [9] M. Monteiro, C. Stari, C. Cabeza, and A. C. Martí, "Magnetic field 'flyby' measurement using a smartphone's magnetometer and accelerometer simultaneously," *Phys. Teach.* 55, 580–581 (2017).
- [10] M. Monteiro, G. Organtini, and A. C. Martí, "Magnetic fields produced by electric railways," *Phys. Teach.* 58, 600–601 (2020).
- [11] K. Forinash and R. F. Wisman, "Smartphones as portable oscilloscopes for physics labs," *Phys. Teach.* 50, 242–243 (2012).
- [12] J. R. Groff, "Estimating RC Time Constants Using Sound," *Phys. Teach.* 57, 393–396 (2019).
- [13] P. Aguilar-Marín, M. Chavez-Bacilio, and S. Jáuregui-Rosas, "Using analog instruments in Tracker video-based experiments to understand the phenomena of electricity and magnetism in physics education," *Eur. J. Phys.* 39, 035204 (2018).
- [14] U. Pili, R. Violanda, and J. Pili, "Using a digital voltmeter and a smartphone camera to investigate the RC circuit," *Phys. Educ.* 54, 033004 (2019).
- [15] N. Westermann, S. Staacks, H. Heinke, and P. Möhrke, "Measuring the magnetic field of a low frequency LC-circuit with phyphox," *Phys. Educ.* 57, 065024 (2022).
- [16] I. Torriente-García, F. M. Muñoz-Pérez, A. C. Martí, M. Monteiro, Juan C. Castro-Palacio, Juan A. Monsoriu, "Experimenting with RC and RL series circuits using smartphones as function generators and oscilloscopes," accepted in *Revista Brasileira de Ensino de Física*.
- [17] Joshua Harden, Amitabh Joshi and Juan D Serna, "Demonstration of double EIT using coupled harmonic oscillators and RLC circuits," *Eur. J. Phys.* 32, 541–558 (2011).

- [18] P. E. Sokol, G. Warren, B. Zheng and P. Smith, "A circuit to demonstrate phase relationships in RLC circuits," *Phys. Educ.* 48 (2013).
- [19] Saša S Ivkovi et al, "LCR circuit: new simple methods for measuring the equivalent series resistance of a capacitor and inductance of a coil," *Eur. J. Phys.* 38 055705 (2017).
- [20] C. E. Mungan, "Simple but accurate driven RLC experiment," *Phys. Educ.* 57, 053002 (2022).
- [21] E. Mathew, S. Karamchandani, and M. T. Biradar, "Mobile Function Generator Using Android," *Procedia Computer Science* 49, 229-234 (2015).
- [22] V. Sotware, "Physics toolbox," (2020), downloaded from Google Play on 1-7-2023.
- [23] S. V. Ballesta, R. Saez, J. Iglesias, and A. Vernet, "Arduino-smartphone device as a physical phenomena measurer," *Phys. Teach.* 58, 663-665 (2020).
- [24] S. Staacks, S. Hütz, H. Heinke, and C. Stampfer, "Measuring the magnetic field of a low frequency LC-circuit with phyphox," *Phys. Educ.* 53, 045009 (2018).